

High True versus Low True

- Binary Boolean Constants are MODELS for Digital Circuit Values
- Can Let 0 Represent False and 1 Represent True – **Positive Logic or High True**
- Can Let 0 Represent True and 1 Represent False – **Negative Logic or Low True**
- Assignment is Arbitrary but Must Know When Building Circuit (**ENCODING**)
- “Bubble Notation” is an Aid to Determine Positive versus Negative Logic

1

High True vs. Low True Logic

- Different ways to say that a signal is **high** true
 - Is high if signal is TRUE, is low if signal is FALSE
 - Is high if signal is 1, is low if signal is 0
 - Is high if signal is *asserted*, is low if signal is *negated* or *deasserted*
- Different ways to say that a signal is **low** true
 - Is low if signal is TRUE, is high if signal is FALSE
 - Is low if signal is 1, is high if signal is 0
 - Is low if signal is *asserted*, is high if signal is *negated* or *deasserted*


2

Asserted vs. Negated

- **Asserted** ALWAYS means that a signal is TRUE
 - Logic 1 could be represented by a HIGH voltage (high true)
 - Logic 1 could be represented by LOW voltage (low true)
- **Negated** (or **Deasserted**) ALWAYS means that a signal is FALSE
 - Logic 0 could be represented by a LOW voltage (low false)
 - Logic 0 could be represented by a HIGH voltage (high false)

3

The Physical World

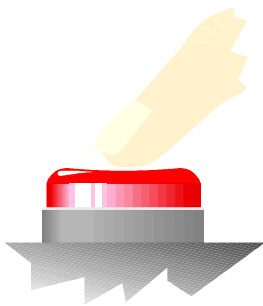


When a button is pressed, it is asserted (true). However, its physical construction may output this as a LOW VOLTAGE (low true)

- Person pressing button doesn't know or care that a low voltage is output
- They just know they have ASSERTED the button


4

Examples of high, low signals

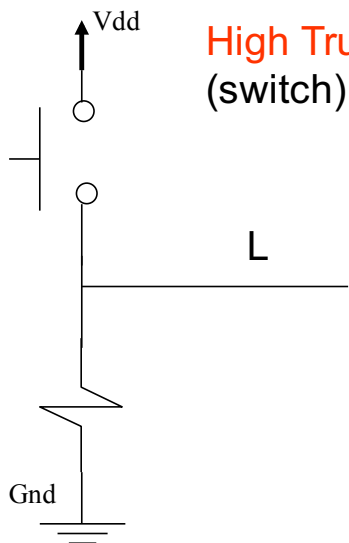

High True button
(switch)


Switch open (negated),
output is L

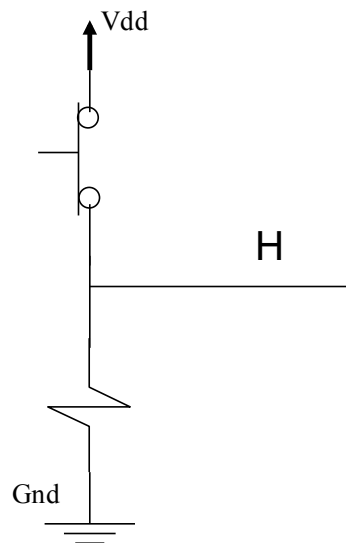

Switch closed
(asserted), output is H


5

Examples of high, low signals

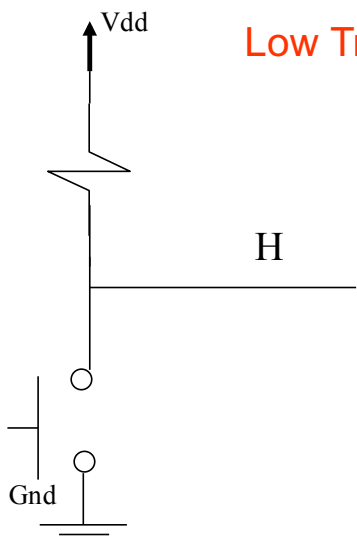

Low True switch

Switch open (negated),
output is H

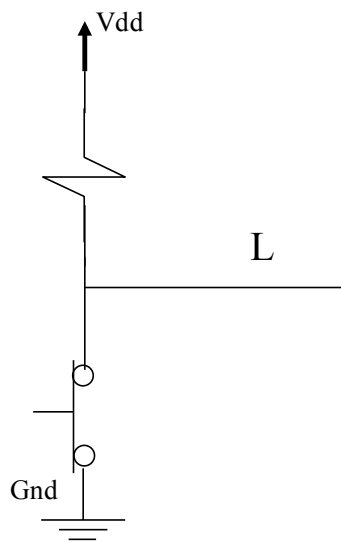


Switch closed
(asserted), output is L

6

7404 Logic Gate

Fixed Logic

A	Y
L	H
H	L

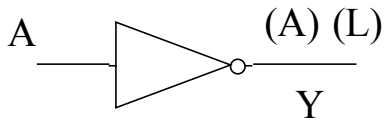


Buffer that converts high true input to low true output

Mixed Logic

A	A (L)
0	0
1	1

A(L)	Y
L	H
H	L

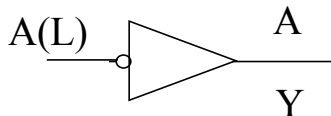

Buffer that converts low true input to high true output

A(L)	A
1	1
0	0



Electronically Identical Circuits – Matter of Interpretation

7

AB	Y
LL	L
LH	L
HL	L
HH	H



TTL Device

7408

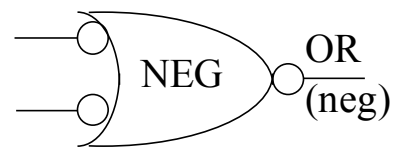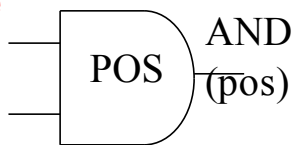

AB	Y
LL	L
LH	H
HL	H
HH	H



7432

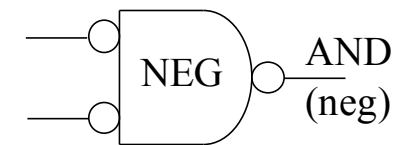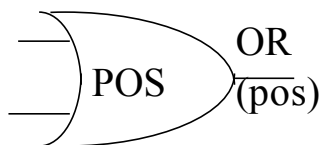

DeMorgan's Theorem



AB	Y
LL	H
LH	H
HL	H
HH	L

7400

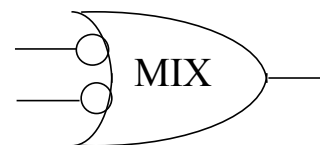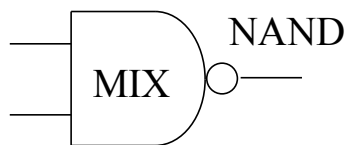

AB	Y
LL	H
LH	L
HL	L
HH	L

7402

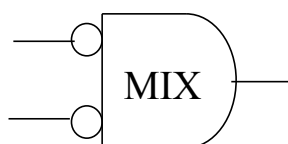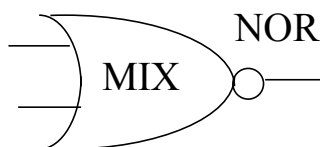


Gate Summaries

8



THE Problem

Have two buttons, each button outputs a low voltage (L) when pressed.

Button A

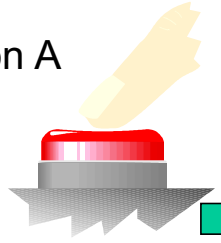

Button B

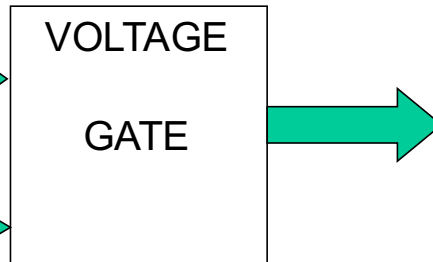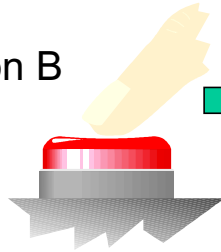


Want a Voltage Gate that outputs a 'H' when both buttons are ASSERTED.

What does the word "both" mean? 9



THE Problem (solution)

Have two buttons, each button outputs a low voltage (L) when pressed.

Button A

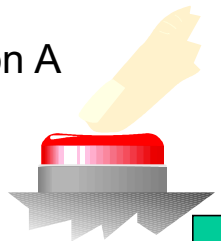


Button B

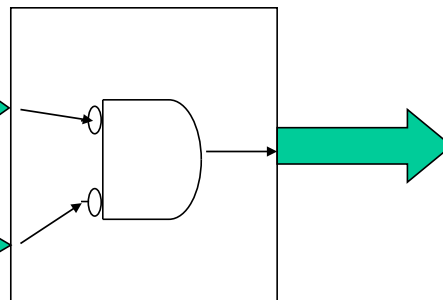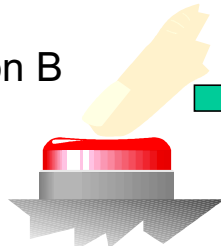

Want a Voltage Gate that outputs a 'H' when both buttons are ASSERTED.


When both A **and** B asserted (low true), output is asserted (high true)

Problem #1

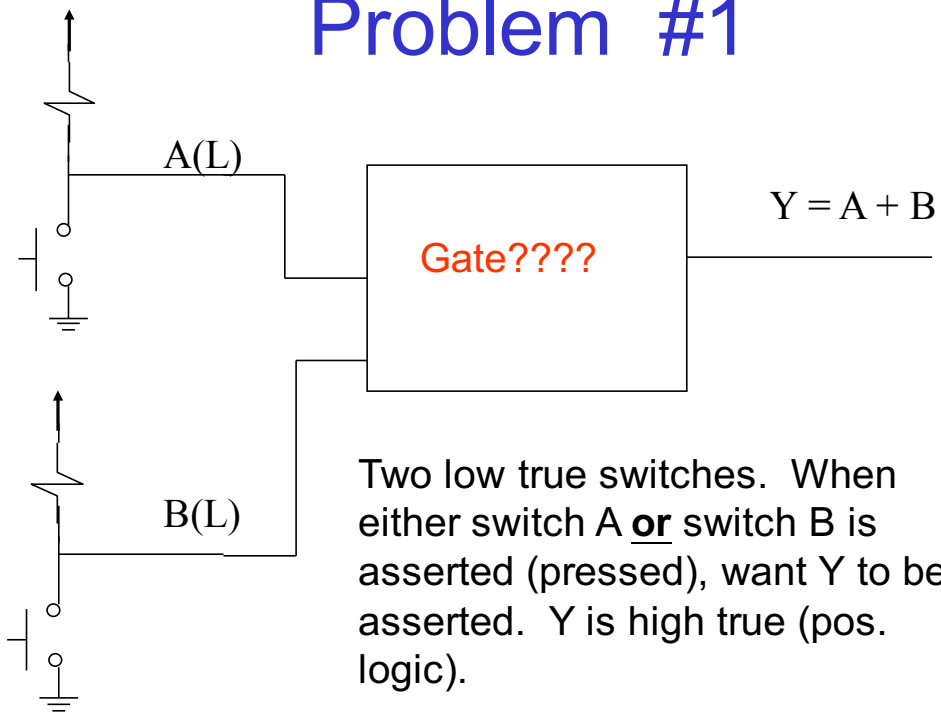


11

Problem #1 (solution)

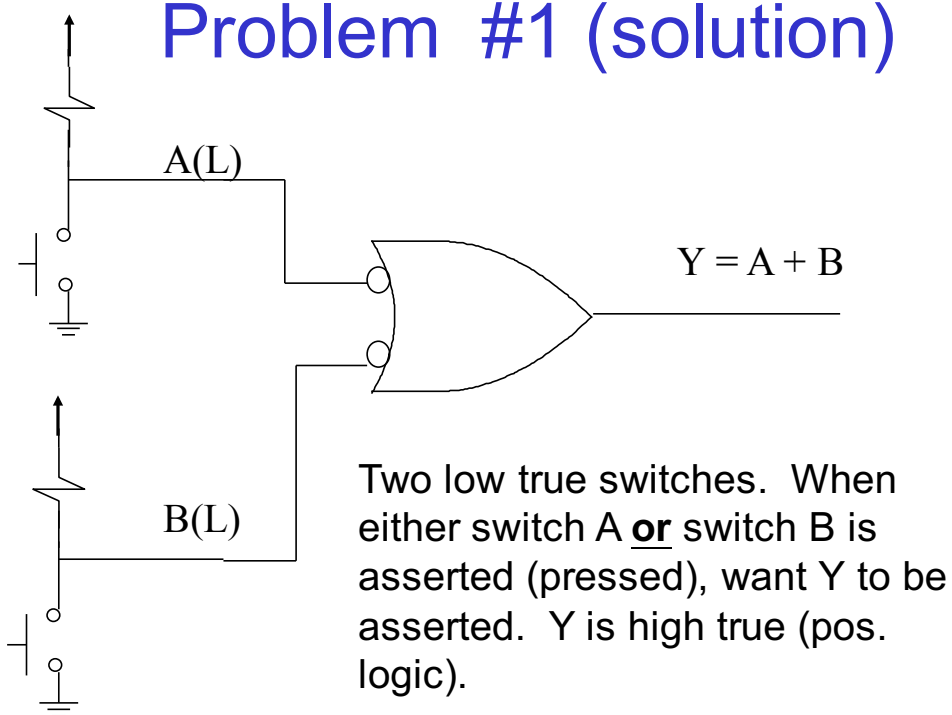


12

Problem #2

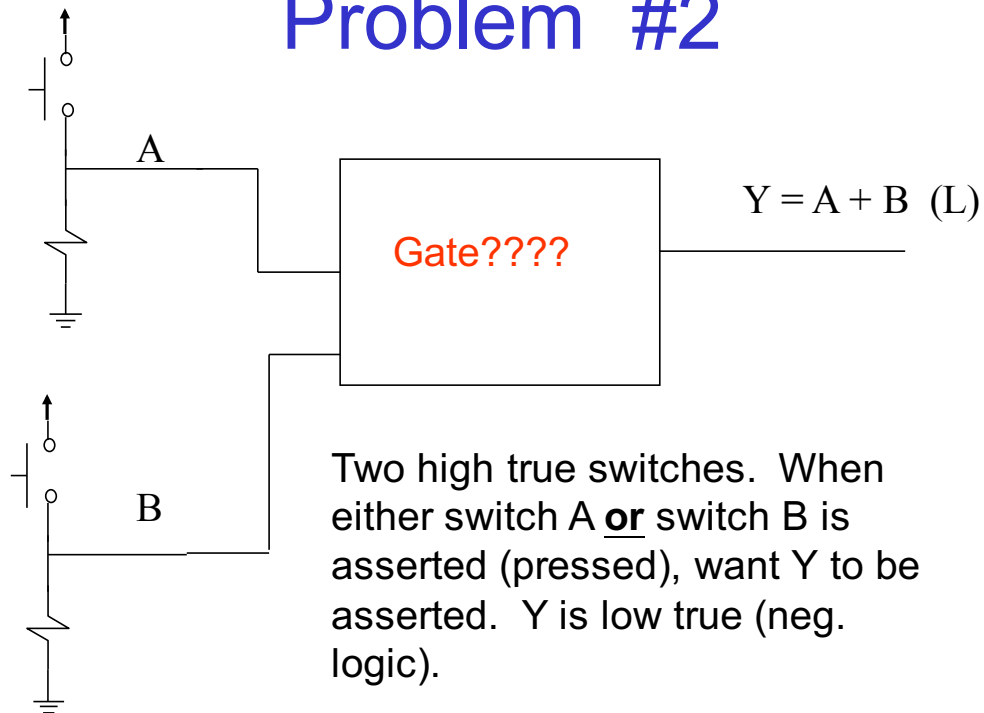


13

Problem #2 (solution)

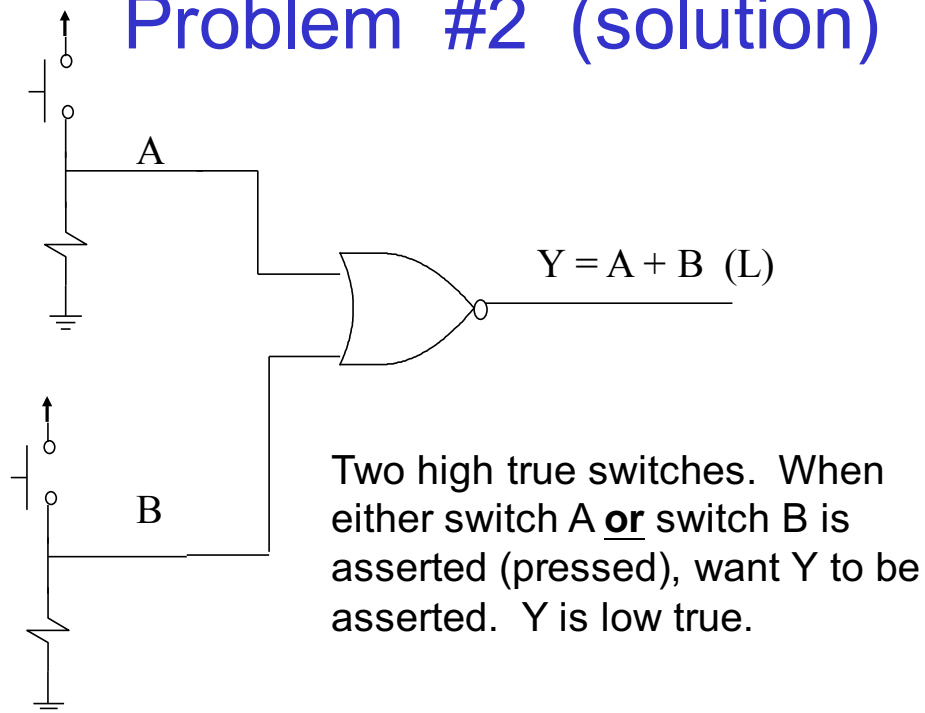


14

Problem #3

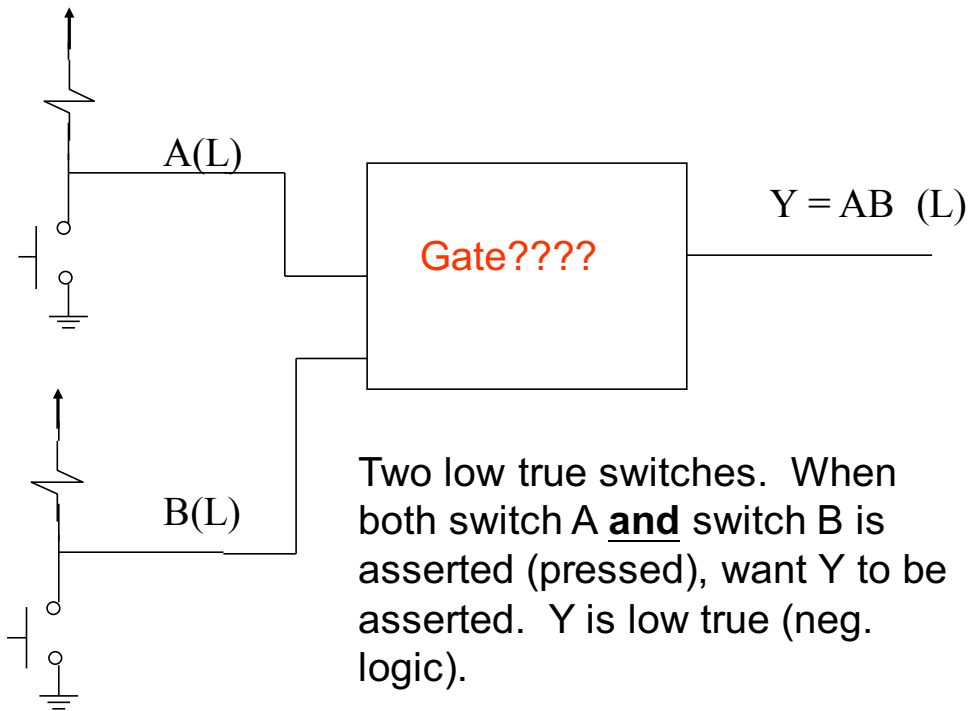


15

Problem #3 (solution)

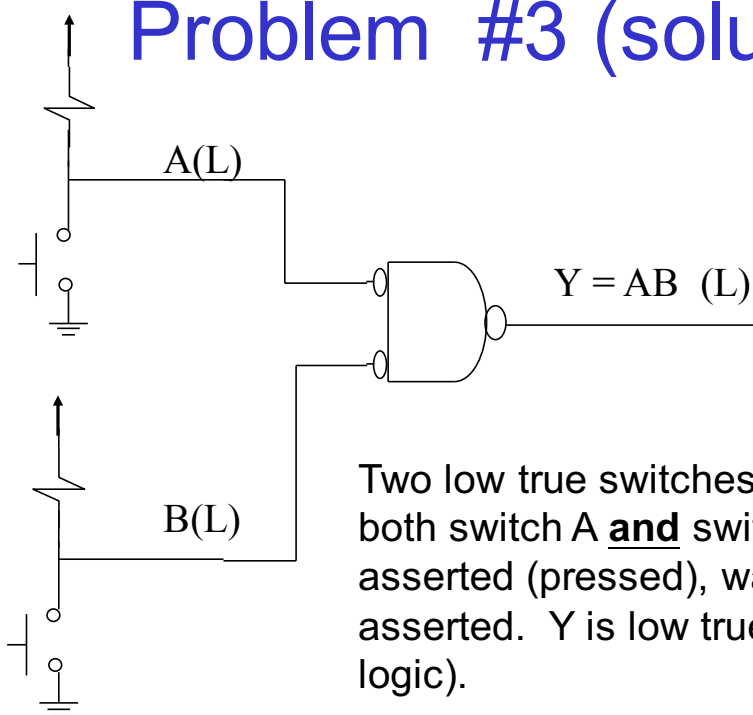


16

Mixed High True, Low True Inputs

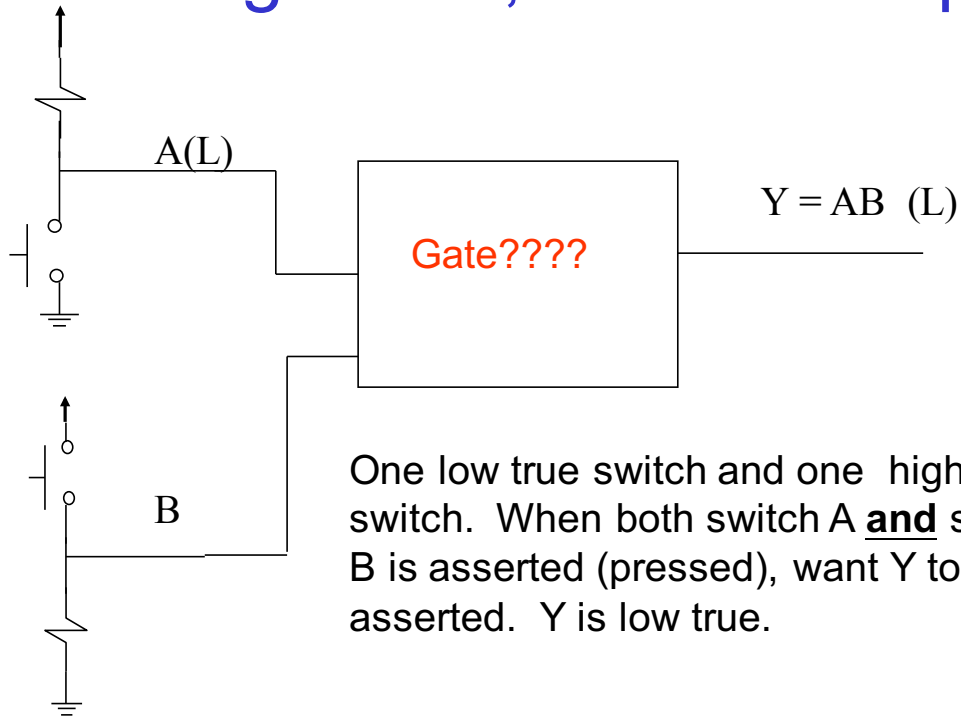


17

Mixed High True, Low True Inputs

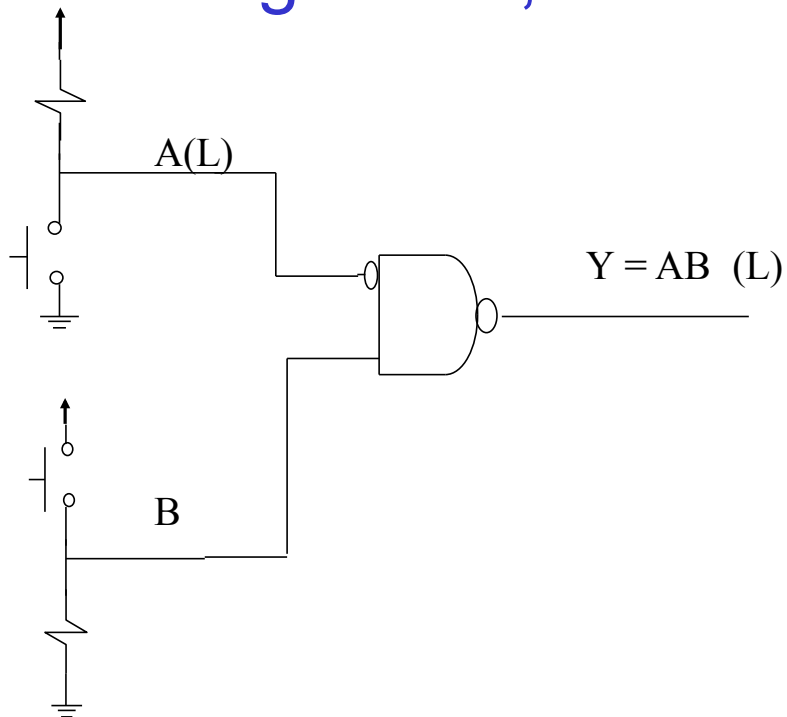


18

Mixed High True, Low True Inputs

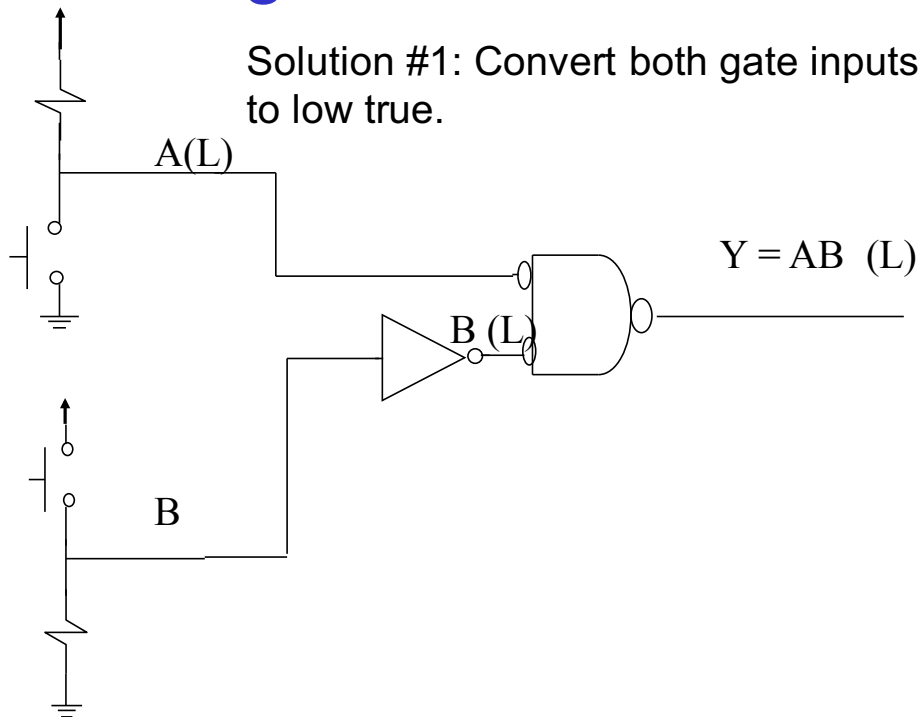


19

Mixed High True, Low True Inputs

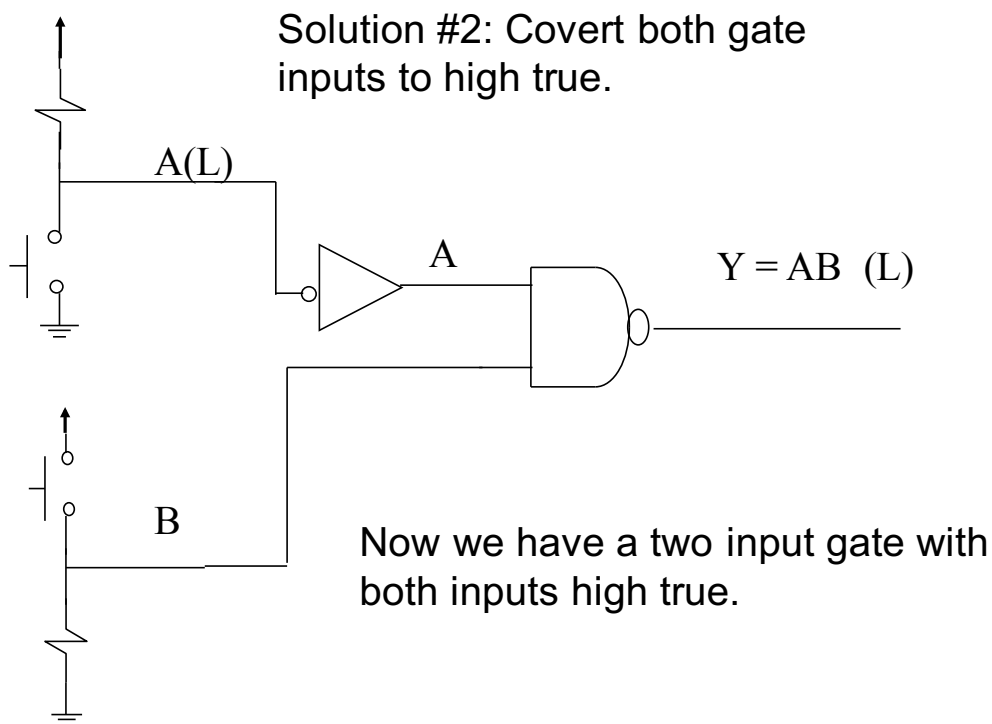


20


Majority Gate (and-or) form

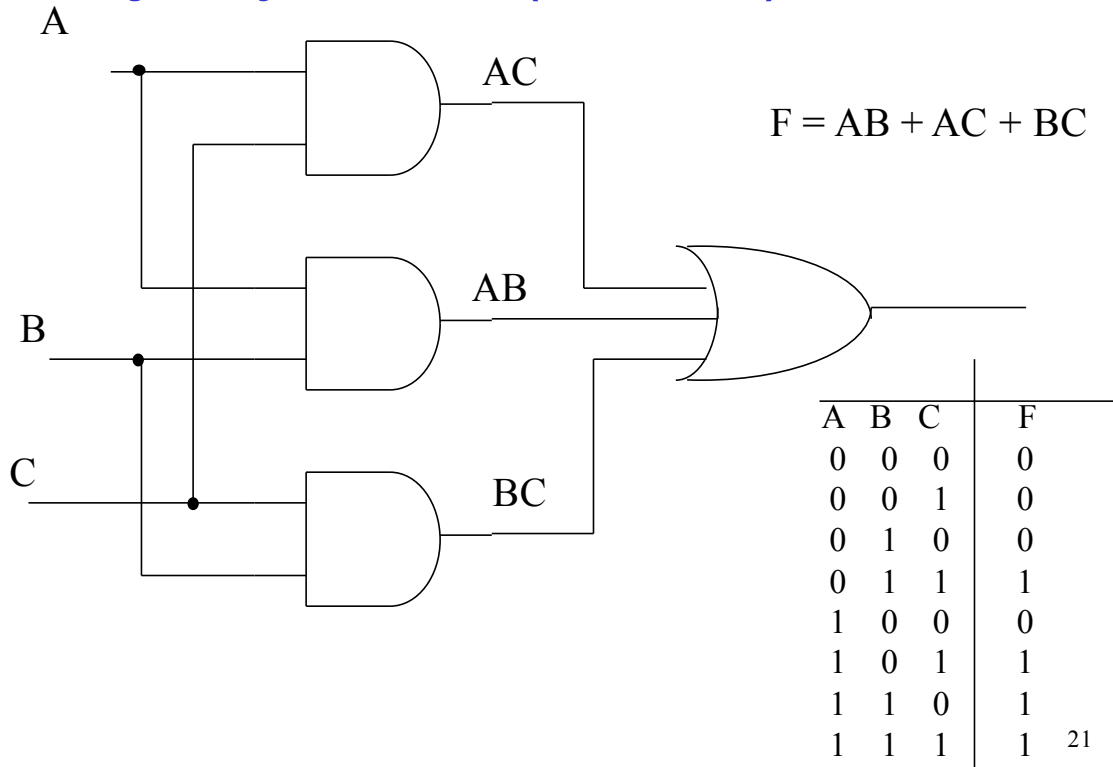

Majority Gate (nand-nand) form

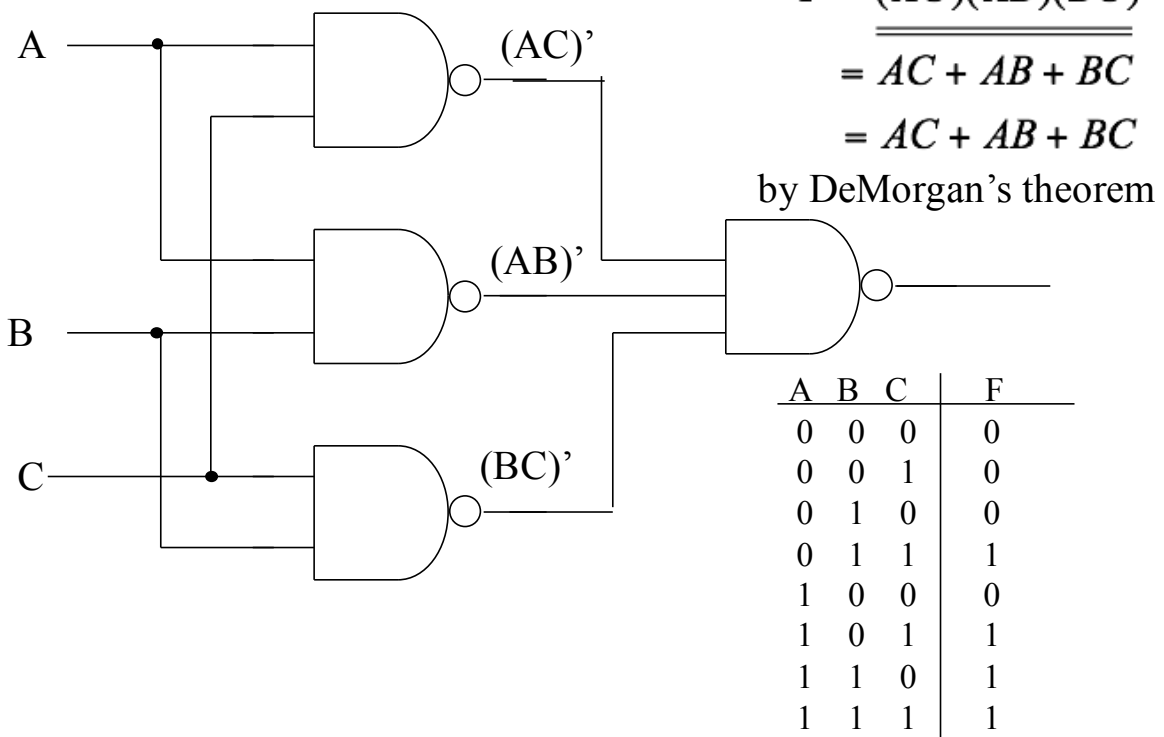

Majority Gate (mixed logic) form

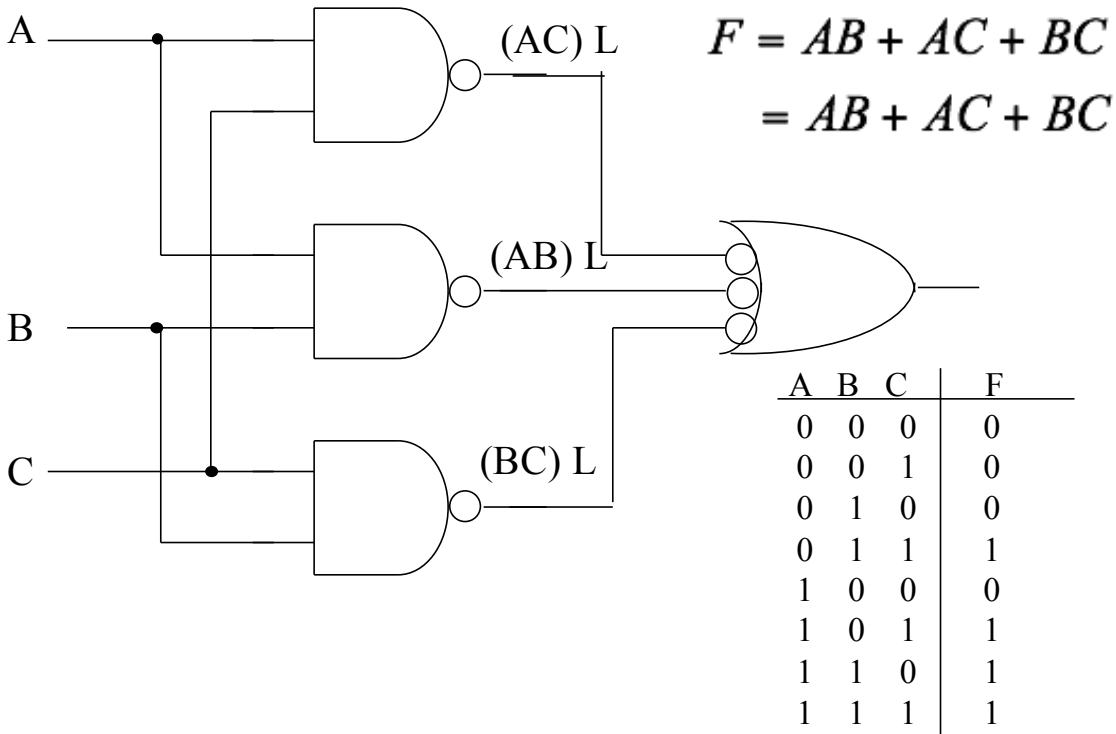

23

Boolean Minimization

Reduce a Boolean equation to fewer terms in SOP form
- hopefully, this will result in using less gates to implement the Boolean equation.

Pencil-Paper: Algebraic techniques, K-maps

Automated: Many powerful algorithms exist

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

$$F = A'BC + AB'C + ABC' + ABC$$

$$F = BC + AC + AB$$

Find Boolean adjacencies to minimize equation; eliminate redundant term

24

Map Method

Graphical Aid for minimization - used to visualize Boolean adjacencies

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

		BC			
		00	01	11	10
A	0	0	0	1	0
	1	0	1	1	1


		BC			
		00	01	11	10
A	0	0	0	1	0
	1	0	1	1	1

$$F = BC + AC + AB$$

25

Boolean Functions to Represent Logic Circuit Behavior


$$f : B^n \rightarrow B^m$$

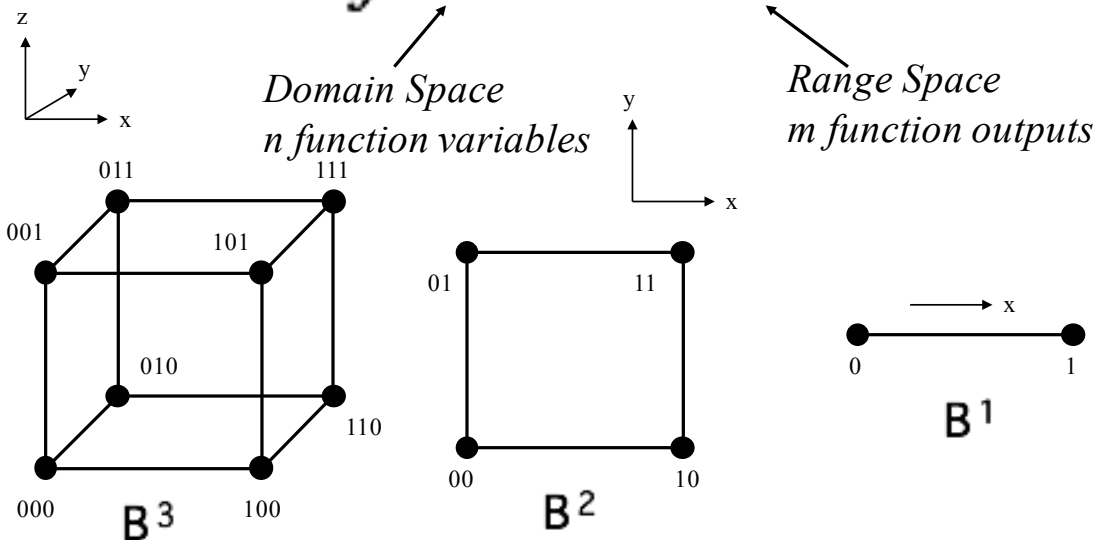

26

Example Boolean Function

$$f : B^3 \rightarrow B^2$$

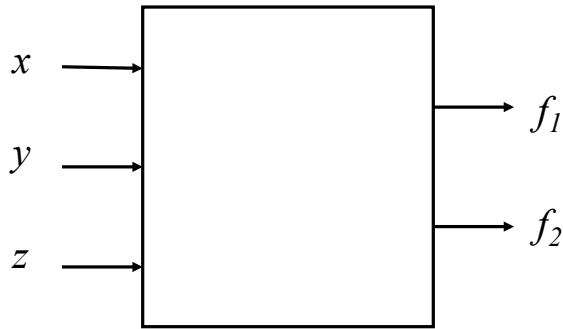


x	y	z	f_1	f_2
0	0	0	0	1
0	0	1	1	1
0	1	0	0	0
0	1	1	1	1
1	0	0	0	1
1	0	1	1	1
1	1	0	1	0
1	1	1	0	1

27

Example Boolean Function


$$f : B^3 \rightarrow B^2$$

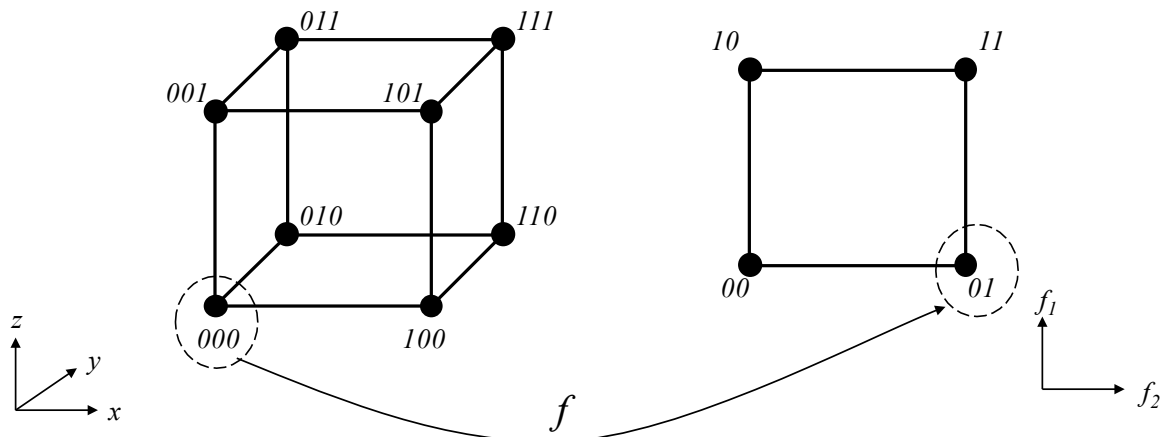

28

Example Boolean Function



(single output function)

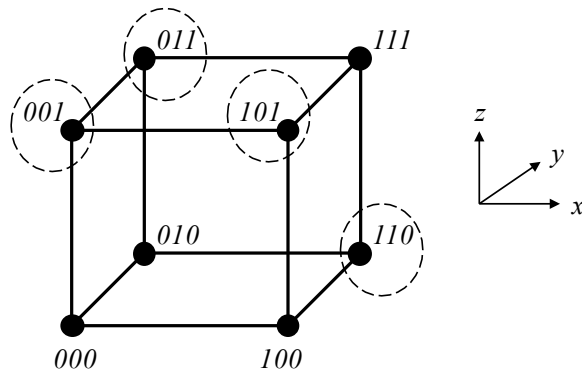

- Represent Function Range by Circling Points in Domain Space
- Each Point is a Cube, B^0
- Each Point is a *minterm* of f_1

29

Combining Cubes

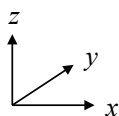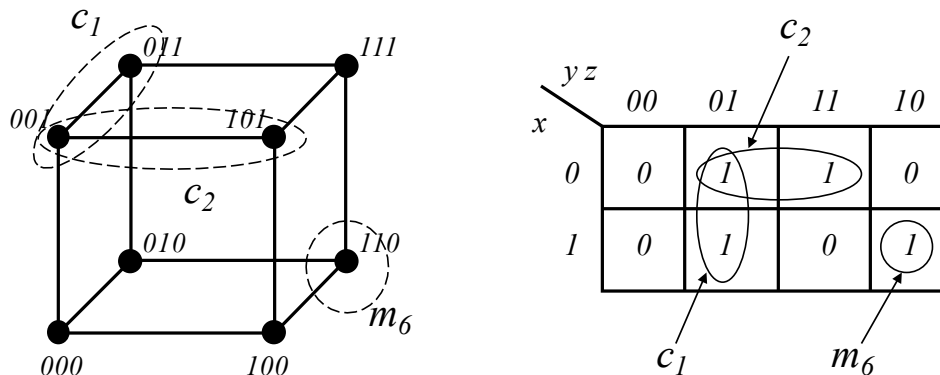

- Adjacent Cubes may be Combined
- Combined Cube has Higher Dimension
- Combined Cube is a *product term*
- This is Same as K-Map Operation

30