


FSM Modeling

- State Diagrams (SDs) and Algorithmic State Machine (ASM) charts Describe Behavior of FSMs
- Translating Directly from SD/ASMs to Verilog is Advantageous
 - No Worry about Mistake in Logic Simplification
 - No Tedious Tables to Create
 - Automatic Tools (synthesis) Create the Schematic Directly
 - Synthesis Tools can Handle Very Large FSMs (100s even 1000s of DFFs)
 - Can EASILY Change State Assignment


Controller Implementation

Will always use HDL to implement controllers in this class.

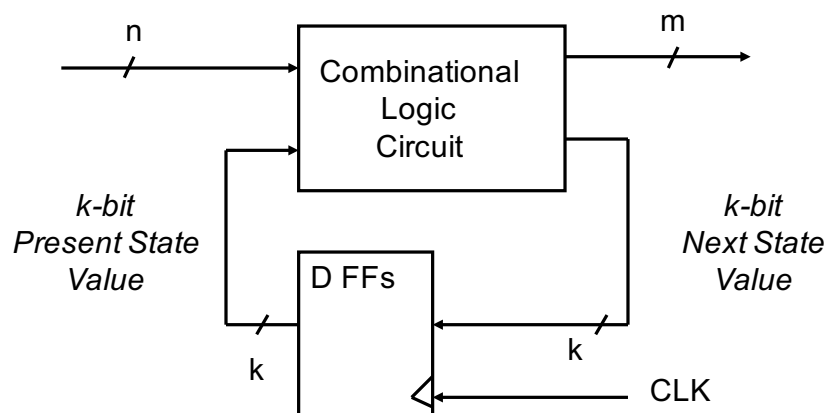A common method is to use ONE block for implementing state registers, ONE block for implementing logic.



Controller Block Diagrams

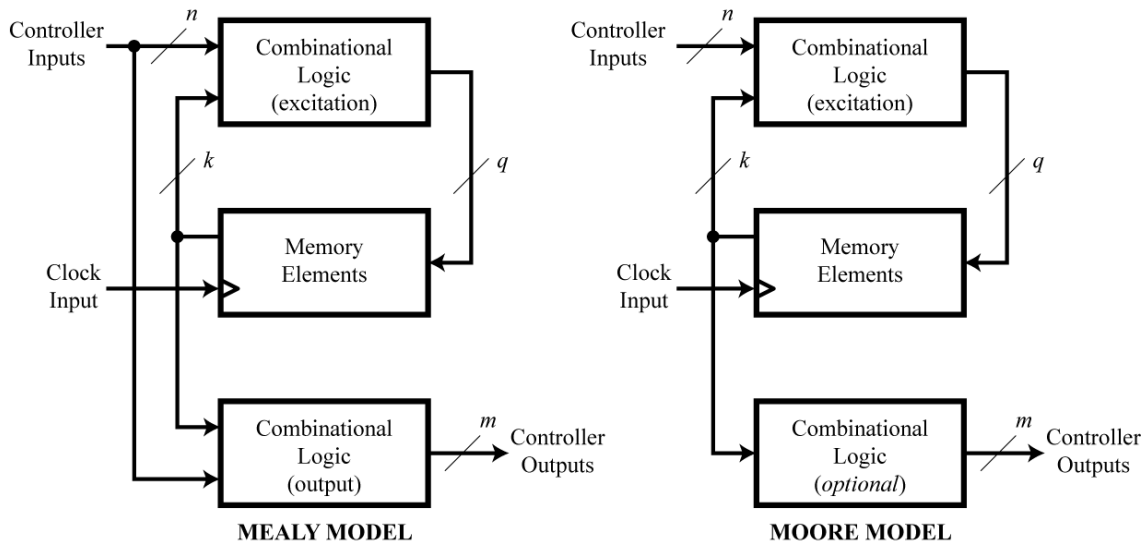

Blocking/Non-blocking Example

- Assume Initially **A=1, B=2, C=3**
- Assume the Following are Within Blocks:

```
B = A;
C = B + 1;
```

Blocking

```
B <= A;
C <= B + 1;
```

Non-Blocking

- When Blocking statements finish Simulation:

A=1, B=1, C=2
- When Non-Blocking statements finish Simulation:

A=1, B=1, C=3

Blocking/Non-blocking Example

- Consider the Following Blocks:

Blocking Statements


```
begin
  A = B;
  B = A;
end
```

Non-Blocking Statements


```
begin
  A <= B;
  B <= A;
end
```

- When Blocking statements finish Simulation:
A and B both end up with the value originally in B
- When Non-Blocking statements finish Simulation:
RHS of assignments first collected into temporary storage
A and B content is interchanged
This gives the effect of concurrency

Synthesis Example

 
 
```
always @ (posedge clk)
begin
  A = Y;
  B = A;
end
```



```
always @ (posedge clk)
begin
  A <= Y;
  B <= A;
end
```


```
always @ (posedge clk)
begin
  B = A;
  A = Y;
end
```

**example from Franzon/Smith book*

Blocking/Non-blocking Rules

- Blocking versus Non-blocking statements can Produce Different Synthesized Circuits
- Use Non-blocking Statements in always Blocks that model Sequential Logic
- Use Blocking Statements in always Blocks that model Combinational Logic
- Do Not Mix Blocking and Non-blocking statements in a Single always Block
- Reasons are Subtle and Have to do with Internal Simulator Queue Scheduling
- Non-adherence to these rules can Lead to Race Conditions or Inference of Incorrect Logic
- See Link to Paper for Details


One always Block Style

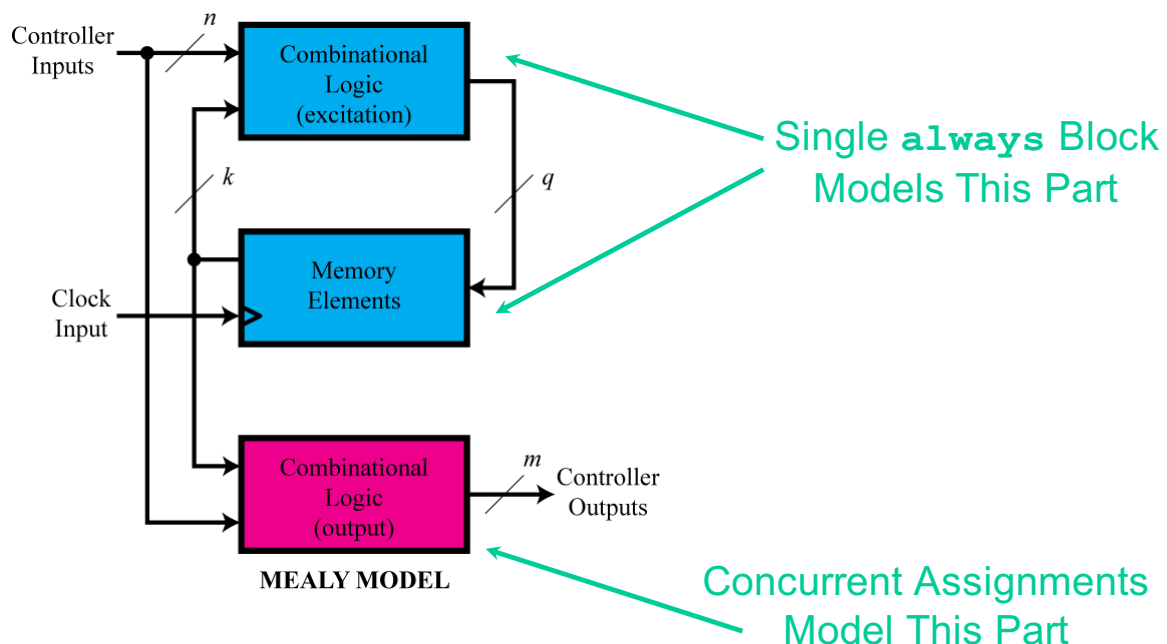

Verilog Controller with Single Always Block (Part 1)

```
module ramfsm_ex1 (state, addr_sel, cnt_en, ld_cnt, zero_we,  
                  set_busy, clr_busy, clk, reset, zero, cnt_eq);  
  input          clk, reset, zero, cnt_eq;  
  output [1:0]  state; //state output for debugging  
  output        addr_sel, cnt_en, ld_cnt, zero_we;  
  output        set_busy, clr_busy;  
  
  reg [1:0] state;  
  
  // State Encoding Here  
  parameter S0=2'b00, S1=2'b01, S2=2'b10;
```

Memory Zeroing ASM Chart

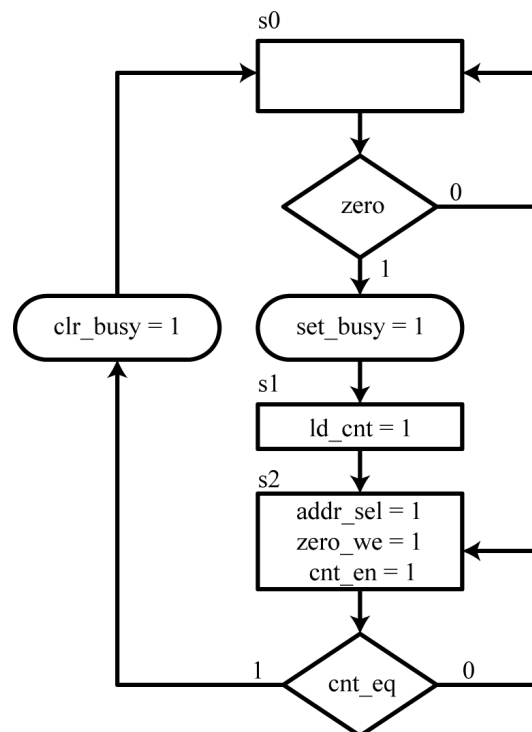

Verilog Controller with Single Always Block (Part 2)

```
// Register and Combinational Transition logic here
always @(posedge clk or posedge reset)
begin
    if (reset == 1'b1)
        state<=S0;
    else
        case (state)
        S0: if (zero == 1'b1) state <= S1;
        S1: state <= S2;
        S2: if (cnt_eq == 1'b1) state <= S0;
        default: state <= S0;
        endcase
    end
// Combinational output logic here
assign set_busy = (state==S0 && zero==1'b1) ? 1'b1 : 1'b0;
assign ld_cnt   = (state==S1) ? 1'b1 : 1'b0;
assign addr_sel = (state==S2) ? 1'b1 : 1'b0;
assign zero_we  = (state==S2) ? 1'b1 : 1'b0;
assign cnt_en   = (state==S2) ? 1'b1 : 1'b0;
assign clr_busy = (state==S2 && cnt_eq==1'b1) ? 1'b1 : 1'b0;

endmodule
```

One Process VHDL Version

```
library ieee;
use ieee.std_logic_1164.all;

-- FSM entity for RAM Zero example
entity ramfsm is
    port ( clk, reset: in std_logic;
          zero, cnt_eq: in std_logic; -- control inputs
          set_busy, clr_busy: out std_logic; -- control outputs
          addr_sel, cnt_en, ld_cnt, zero_we: out std_logic;
          state: out std_logic_vector(1 downto 0) -- state out for
debugging
    );

end ramfsm;

architecture a of ramfsm is
    signal pstate: std_logic_vector(1 downto 0);
    -- state encoding
    CONSTANT S0 : std_logic_vector(1 downto 0) := "00";
    CONSTANT S1 : std_logic_vector(1 downto 0) := "01";
    CONSTANT S2 : std_logic_vector(1 downto 0) := "10";
```

One Process VHDL Version (cont)


```
begin
  state <= pstate;           -- look at present state for debugging
  purposes
  stateff:process(clk)      -- process has state transistions ONLY
  begin
    if (reset = '1') then  pstate <= S0;
    elsif (clk'event and clk='1') then -- rising edge of clock
      CASE pstate IS
        WHEN S0 =>  if (zero = '1') then  pstate <= S1;  end if;
        WHEN S1 =>  pstate <= S2;
                    WHEN S2 =>  if (cnt_eq = '1') then pstate <=
S0 ;  end if;
                    WHEN others => pstate <= S0;
      end case;
    end if;
  end process stateff;

  set_busy <= '1' when (pstate = S0 and zero = '1') else '0';
  ld_cnt <= '1' when (pstate = S1) else '0';
  addr_sel <= '1' when (pstate = S2) else '0';
  zero_we <= '1' when (pstate = S2) else '0';
  cnt_en <= '1' when (pstate = S2) else '0';
  clr_busy <= '1' when (pstate = S2 and cnt_eq = '1') else '0';
end a;
```

Comments on One always Block Implementation

- **always** block defines state FFs and transitions between states
- Outputs of controller are separate concurrent statements outside of synchronous block
- Can be confusing since you separate out the FSM outputs from their state definitions within the CASE statement

Two always Blocks Style

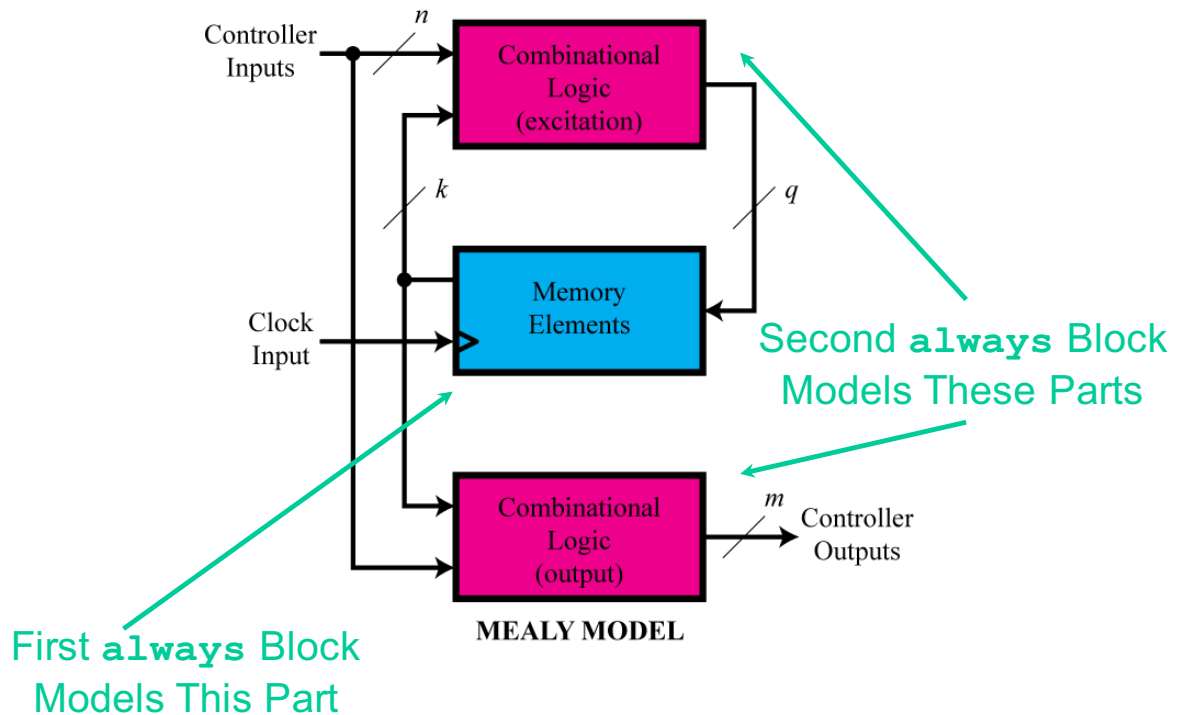

Controller Verilog with Two Always Blocks (Part 1)

```
module ramfsm_ex2 (pstate, addr_sel, cnt_en, ld_cnt, zero_we,
    set_busy, clr_busy, clk, reset, zero, cnt_eq);
    input      clk, reset, zero, cnt_eq;
    output [1:0] pstate; //state output for debugging
    output     addr_sel, cnt_en, ld_cnt, zero_we;
    output     set_busy, clr_busy;
    reg        addr_sel, cnt_en, ld_cnt, zero_we, set_busy, clr_busy;
    reg [1:0] pstate, nstate;

    // State Encoding Here
    parameter S0=2'b00, S1=2'b01, S2=2'b10;

    // Register logic here
    always @(posedge clk or posedge reset)
    begin
        if (reset == 1'b1) pstate <= S0;
        else pstate <= nstate;
    end
end
```


Controller Verilog with Two Always Blocks

(Part 2)

```
// Combinational transition and output logic here
always @(pstate or zero or cnt_eq)
  begin
    // We must include default values here
    // to avoid inferred latches
    set_busy = 1'b0;
    ld_cnt   = 1'b0;
    clr_busy = 1'b0;
    addr_sel = 1'b0;
    zero_we  = 1'b0;
    cnt_en   = 1'b0;

// Transition and output logic in case statement
    case (pstate)
      S0: if (zero == 1'b1)
          begin
            nstate = S1;
            set_busy = 1'b1;
          end
        else nstate = S0;
```

Controller Verilog with Two Always Blocks

(Part 3)

```
S1: begin
  nstate = S2;
  ld_cnt = 1'b1;
end
S2: begin
  if (cnt_eq == 1'b1)
    begin
      nstate = S0;
      clr_busy = 1'b1;
    end
  else nstate = S2;
  addr_sel = 1'b1;
  zero_we  = 1'b1;
  cnt_en   = 1'b1;
end
default: nstate = S0;
endcase
end
endmodule
```

Two Process VHDL Version

```
architecture a of ramfsm is
  signal pstate, nstate: std_logic_vector(1 downto 0);
  -- state encoding
  CONSTANT S0 : std_logic_vector(1 downto 0) := "00";
  CONSTANT S1 : std_logic_vector(1 downto 0) := "01";
  CONSTANT S2 : std_logic_vector(1 downto 0) := "10";

begin
  state <= pstate;          -- look at present state for debugging
  purposes

  stateff:process(clk)     -- process has DFFs only
  begin
    if (reset = '1') then  pstate <= S0;
    elsif (clk'event and clk='1') then
      pstate <= nstate;    -- update pres. w. next state
    endif;
  end process stateff;
end architecture a;
```


Two Process VHDL Version

```
comblogic: process (zero, cnt_eq, pstate)
begin
  -- default assignments
  nstate <= pstate;
  set_busy <= '0'; clr_busy <= '0';
  ld_cnt <= '0';
  addr_sel <= '0';
  zero_we <= '0';
  cnt_en <= '0';
  CASE pstate IS
    WHEN S0 => if (zero = '1') then
      set_busy <= '1'; nstate <= S1;
    end if;
    WHEN S1 => ld_cnt <= '1'; nstate <= S2;
    WHEN S2 => zero_we <= '1';
      cnt_en <= '1'; addr_sel <= '1';
      if (cnt_eq = '1') then
        clr_busy <= '1'; nstate <= S0 ;
      end if;
    WHEN others => nstate <= S0;
  end case;
end if;
end process comblogic;
end a;
```

Comments on Two always block Implementation

- First **always** block process defines only FFs
- Second **always** block defines
 - State transitions
 - Output assertions
 - Has natural mapping from ASM chart to CASE statement
- Default assignments to outputs in Combinational **always** Block (VHDL Comblogic process) very important to Prevent Inferred Latches

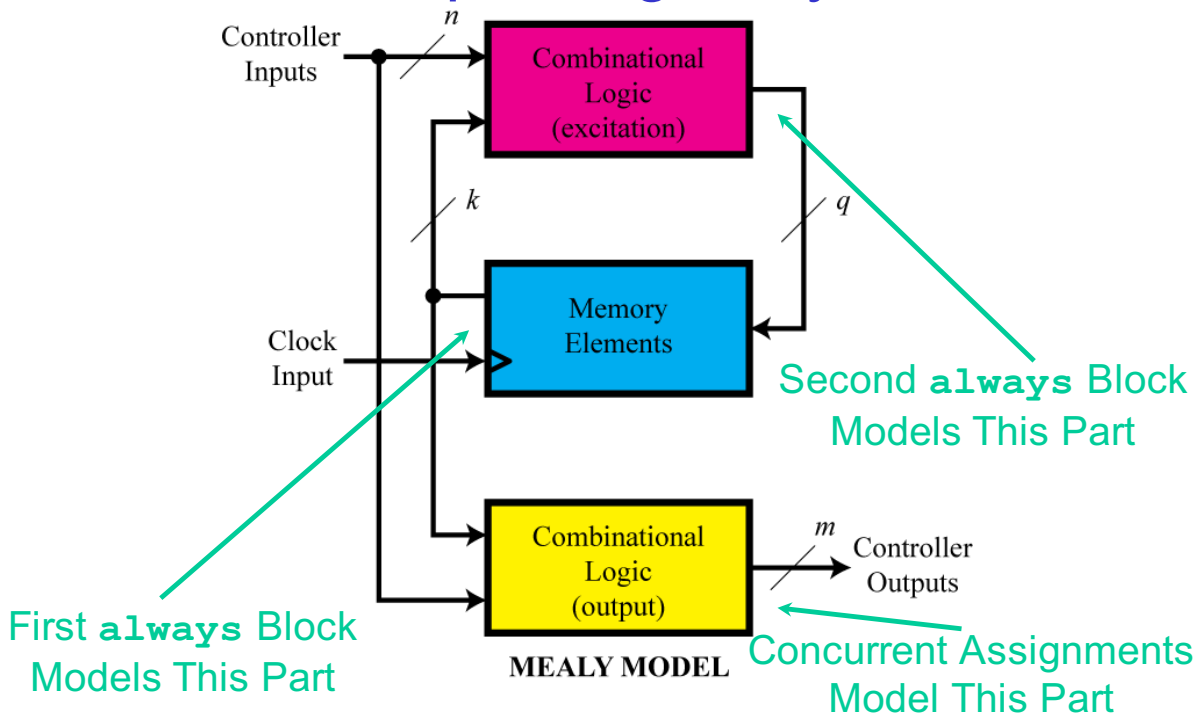Two always Blocks with Concurrent Output Logic Style



Controller Verilog with Two Always Blocks and Concurrent Logic (Part 1)

```
module ramfsm_ex3 (pstate, addr_sel, cnt_en, ld_cnt, zero_we,
                  set_busy, clr_busy, clk, reset, zero, cnt_eq);
  input          clk, reset, zero, cnt_eq;
  output [1:0] pstate; //state output for debugging
  output        addr_sel, cnt_en, ld_cnt, zero_we;
  output        set_busy, clr_busy;
  reg   [1:0] pstate, nstate;

  // State Encoding Here
  parameter S0=2'b00, S1=2'b01, S2=2'b10;

  // Register logic here
  always @(posedge clk or posedge reset)
  begin
    if (reset == 1'b1) pstate<=S0;
    else pstate <= nstate;
  end
end
```

Controller Verilog with Two Always Blocks and Concurrent Logic (Part 2)


```
// Combinational transition logic here
always @(pstate)
begin
  case (pstate)
    S0: if (zero == 1'b1)
        nstate = S1;
        else
        nstate = S0;
    S1: nstate = S2;
    S2: if (cnt_eq == 1'b1)
        nstate = S0;
        else
        nstate = S2;
    default: nstate = S0;
  endcase
end
```

Controller Verilog with Two Always Blocks and Concurrent Logic (Part 3)


```
// Combinational output logic here
assign set_busy  = (pstate==S0 && zero==1'b1) ? 1'b1 : 1'b0;
assign ld_cnt    = (pstate==S1) ? 1'b1 : 1'b0;
assign addr_sel  = (pstate==S2) ? 1'b1 : 1'b0;
assign zero_we   = (pstate==S2) ? 1'b1 : 1'b0;
assign cnt_en    = (pstate==S2) ? 1'b1 : 1'b0;
assign clr_busy  = (pstate==S2 && cnt_eq==1'b1) ? 1'b1 : 1'b0;

endmodule
```


FSM Timing: Start Zero Operation

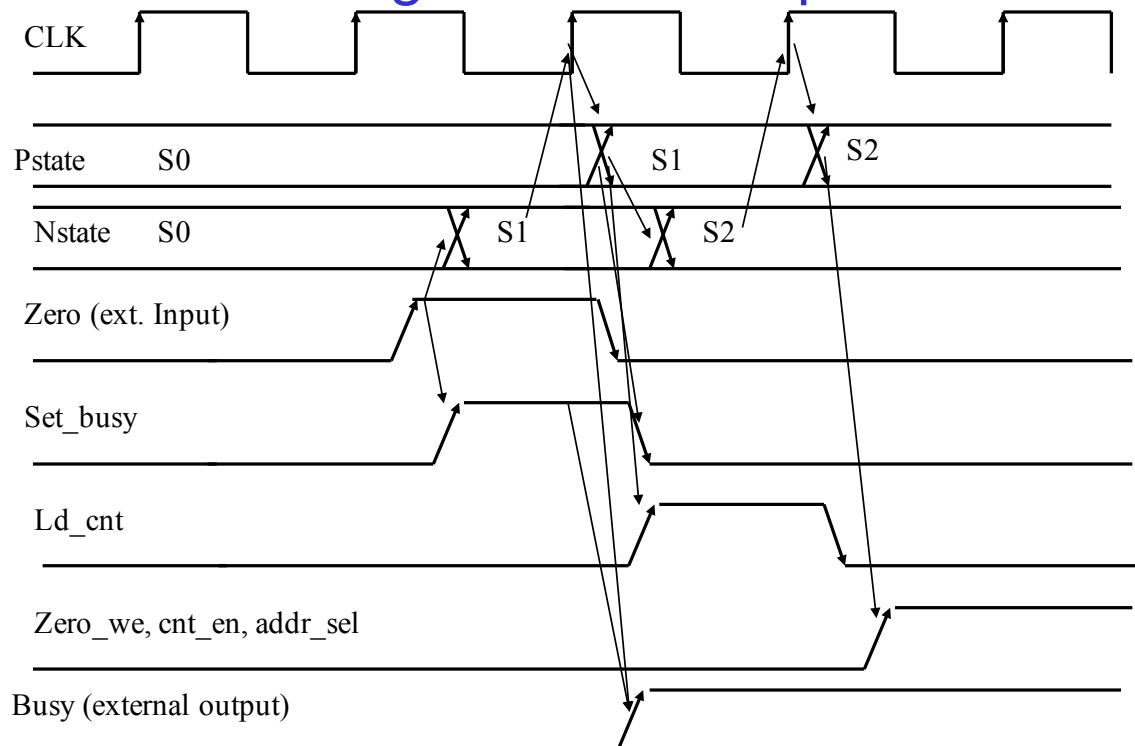

FSM Timing: Finish Zero Operation

 

Controller Block Diagrams

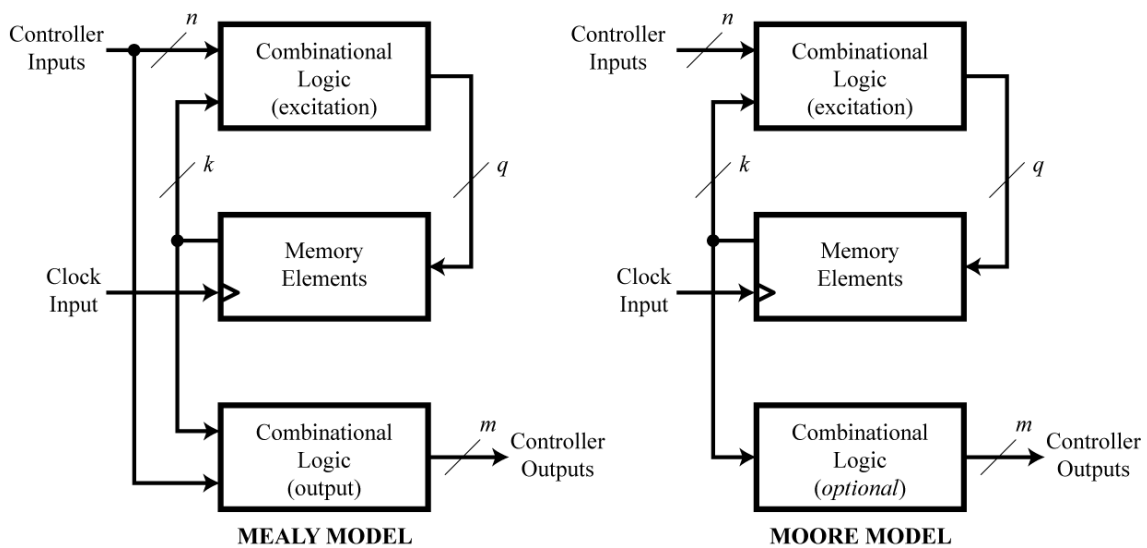


Comments

- Note that **pstate** changes on active clock edge
- Conditional outputs will change based on present state AND external inputs
- Unconditional outputs change on clock edge and remain true as long as in the current state
- In order for **busy** to go high in State **s1**, '**set_busy**' must be asserted in **s0** since **busy** comes from JK FF.

Comments

- Note that for **busy** to go low in **s0**, then "**clr_busy**" had to be asserted in State **s2**.
- Note that the '**cnt_en**' signal stays true for one clock edge after '**cnt_eq**' goes true
 - This means that the COUNTER will increment to HIGH+1, sometimes this makes a difference, need to be aware of it


Synthesized Controller Logic

 

Mealy versus Moore


- Previous 3 Styles of Controller HDL Synthesize to Circuitry with Identical Input/Output Behavior
- Can Transform Mealy Model to Moore Model
- Timing Behavior Changes Since Outputs Change Only at Clock Edges
- May or May Not be Desirable to Utilize a Moore Model Implementation

Memory Zeroing State Diagram

 


Mealy Controller Model

Mealy to Moore Conversion

 


Memory Zeroing State Diagram

Symbolic States

 


State Values Assigned in Bold

 

Moore Controller Model

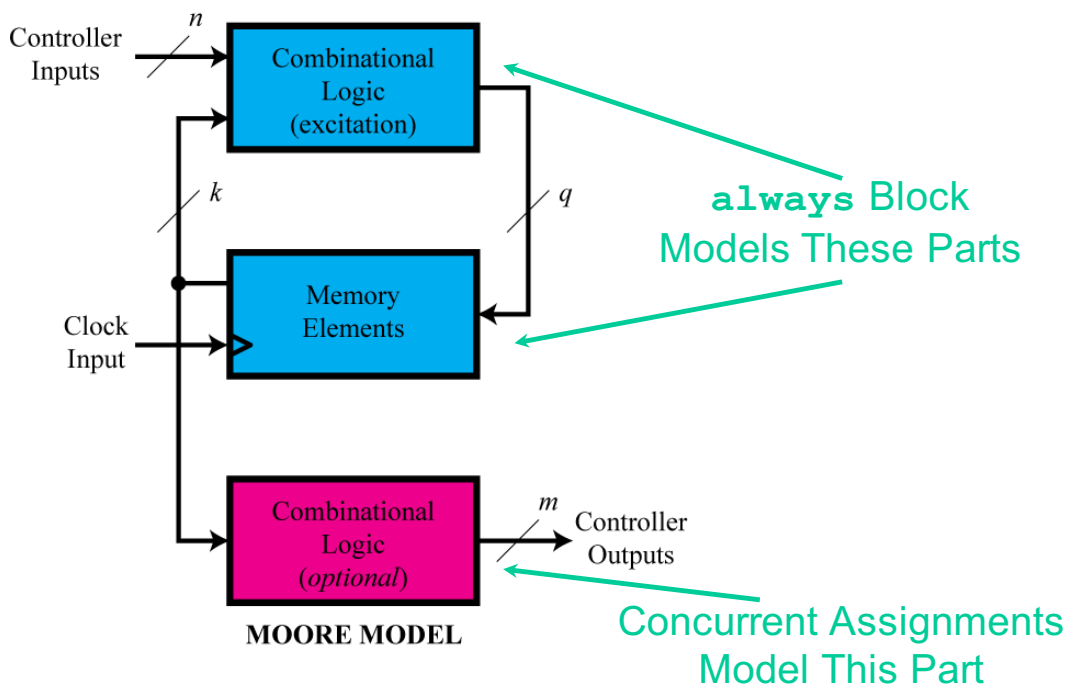One always Block with Concurrent Output Logic Style



Controller Verilog Implemented as Moore Machine (Part 1)

```
module ramfsm_ex4 (state, addr_sel, cnt_en, ld_cnt,
                  zero_we, set_busy, clr_busy, clk,
                  reset, zero, cnt_eq);
    input          clk, reset, zero, cnt_eq;
    output [6:0] state; //state output for debugging
    output        addr_sel, cnt_en, ld_cnt, zero_we;
    output        set_busy, clr_busy;

    reg    [6:0] state;

    // State Encoding Here
    parameter A=7'b0000000, B=7'b0101000, C=7'b0000111,
              D=7'b1000111 , E=7'b0010000;
```

Controller Verilog Implemented as Moore Machine (Part 2)

```
// Register and Combinational Transition logic here
always @(posedge clk or posedge reset)
    begin
        if (reset == 1'b1)
            state<=A;
        else
            case (state)
            A: if (zero == 1'b1)
                state <= B;
                else
                    state <= A;
            B: state <= C;
            C: state <= D;
```

Controller Verilog Implemented as Moore Machine (Part 3)

```
D: if (cnt_eq == 1'b1)
        state <= E;
    else
        state <= D;
D: state <= E;
E: state <= A;
default: state <= A;
endcase

end
```

Controller Verilog Implemented as Moore Machine (Part 4)

```
// Outputs are directly the state
// encoding signals
assign set_busy = state[5];
assign clr_busy = state[4];
assign ld_cnt = state[3];
assign addr_sel = state[2];
assign zero_we = state[1];
assign cnt_en = state[0];
endmodule
```

Verilog Coding Guidelines

1. Use blocking assignments (“=”) in **always** blocks that are meant to represent combinational logic.
2. Use non-blocking assignments (“<=”) in **always** blocks that are meant to represent sequential logic.
3. Do not mix blocking and non-blocking assignments in the same **always** block. If an **always** block contains a significant amount of combinational logic that requires intermediate wires (and thus, intermediate assignments), then place this logic in a separate **always** block.

Verilog Coding Guidelines (Cont.)

4. If an **always** block for combinational logic contains complicated logic pathways due to *if-else* branching or other logic constructs, then assign every output a default value at the beginning of the block. This ensures that all outputs are assigned a value regardless of the path taken through the logic, avoiding inferred latches on outputs.
5. Do not make assignments to the same output from multiple **always** blocks.

Synthesis Tool Warnings

"Input X is unused (does not drive any logic)"

- This means that the synthesized logic does not make use of a particular input.

"Output X is stuck at VDD (or GND)"

- This means that in the synthesized logic there is an output that has been reduced to a fixed '1' or '0' with no gating.

"Outputs X and Y share the same net"

- This means that the logic for outputs **X** and **Y** is the same, and that outputs **X** and **Y** are driven by the same gate.

Synthesis Tool Warnings (cont)

"Output X has no driver"

- This means that an output has never been assigned, and thus no logic has been synthesized to drive it.


"Combinational loop detected on net X"

- This means that the synthesis tool has found a feedback path from a combinational gate output back to one of its inputs without an intervening latch or DFF.
- Unless an *asynchronous* (i.e, no clock is used) digital system is being designed, this is an error in coding as all feedback paths should be broken by a sequential element.


Combinational Loops

(a) A combinational loop

```
always @*
begin
  y = y + a;
end
```

 


 Output oscillates; period is dependent upon adder delay




 (b) Sequential element in feedback path

```
always @(posedge clk)
begin
  y <= y + a;
end
```



 Output can only change on the active clock edge




3 `always` Blocks FSM Modeling Approach

- Basic Construct is `case` Statement within an `always` Block
- Can Internally Keep two `regs`, `Prstate` and `Nxtstate`
- Use Three `always` blocks (another way to do it)
 - Interact by causing events in different blocks
 - first `always` block handles asynchronous and synchronous events
 - second `always` block determines the next state
 - third `always` block evaluates output signals

Verilog FSM Behavioral Model Example

Mealy Machine

 

© 2002 Prentice Hall, Inc.
M. Morris Mano
DIGITAL DESIGN, 3e.

Fig. 5-16 State Diagram of the Circuit of Fig. 5-15

Verilog FSM Model Example

```

//HDL Example 5-5 (adapted-MAT)
//-----
//Mealy state diagram (Fig 5-16)
module Mealy_md1 (x,y,CLK,RST);
  input x,CLK,RST;
  output y;
  reg y;
  reg [1:0] Prstate, Nxtstate;
  parameter S0 = 2'b00, S1 = 2'b01, S2 = 2'b10, S3 = 2'b11;
  always @ (posedge CLK or negedge RST) // Clocked block
    if (~RST) Prstate <= S0; //Initialize to state S0
    else Prstate <= Nxtstate; //Clock operations
  always @ (Prstate or x) //Determine next state
    case (Prstate) //Transition Functions
      S0: if (x) Nxtstate = S1;
      S1: if (x) Nxtstate = S3;
           else Nxtstate = S0;
      S2: if (~x)Nxtstate = S0;
      S3: if (x) Nxtstate = S2;
           else Nxtstate = S0;
    endcase
endmodule
  
```

© 2002 Prentice Hall, Inc.
M. Morris Mano
DIGITAL DESIGN, 3e.


Verilog FSM Behavioral Model Example

```
always @ (Prstate or x)      //Evaluate output
  case (Prstate)             //Output Functions
    S0: y = 0;
    S1: if (x) y = 1'b0; else y = 1'b1;
    S2: if (x) y = 1'b0; else y = 1'b1;
    S3: if (x) y = 1'b0; else y = 1'b1;
  endcase
endmodule
```

© 2002 Prentice Hall, Inc.
M. Morris Mano
DIGITAL DESIGN, 3e.

Verilog FSM Behavioral Model Example

Moore Machine

 

Verilog FSM Behavioral Model Example

Moore Machine

```
//HDL Example 5-6 (adapted-MAT)
//-----
//Moore state diagram (Fig. 5-19)
module Moore_md1 (x,AB,CLK,RST);
  input x,CLK,RST;
  output [1:0]AB;
  reg [1:0] state;
  parameter S0 = 2'b00, S1 = 2'b01, S2 = 2'b10, S3 = 2'b11;
  always @ (posedge CLK or negedge RST)
    if (~RST) state <= S0; //Initialize to state S0
    else // Clocked block and Transition Logic
      case (state)
        S0: if (~x) state <= S1; else state <= S0;
        S1: if (x) state <= S2; else state <= S3;
        S2: if (~x) state <= S3; else state <= S2;
        S3: if (~x) state <= S0; else state <= S3;
      endcase
  assign AB = state; //Output Function
endmodule
```