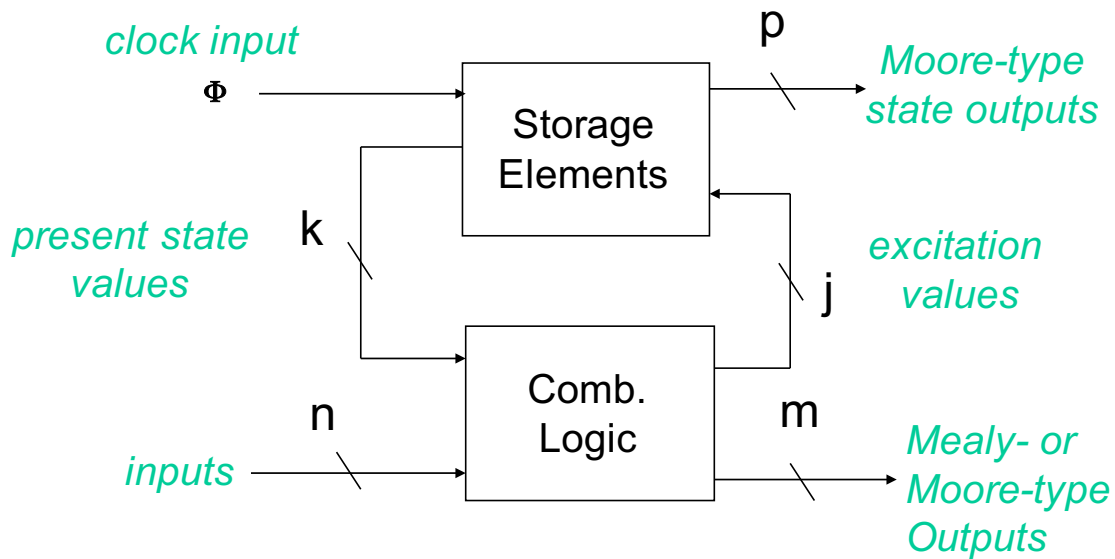


State Assignment (Encoding)



- Encode State Vectors to Enhance Logic Area and Performance

State Encoding Motivation

- FUNCTIONALITY
 - Glitches Can Cause Problems During Transitions
 - Especially when Driving Output Control Signals (Use Synchronous Inputs on Datapath Elements if Possible!!!!)
- AREA
 - Want the Transition Logic to be Minimal in Total Number of Transistors
- SPEED
 - Want Combinational Logic *Maximum Delay Path* to be Small
 - Does Small Logic Path = Small Delay ?????
NO – NOT NECESSARILY – FAN-IN DEPENDENCE ALSO!!!!
- POWER
 - CMOS is Predominant Implementation Logic Style
 - More Switching Leads to Current Increase
 - Less Switching can lead to Decreased Dynamic Power Dissipation

Example Controller (GLITCH)

```
module contrlr1 (state, ld_xi, iterate, cnt_ld,
                 cnt_en, busy, ld_b, done, clk, reset);
    input        clk, reset, ld_b, done;
    output       ld_xi, iterate, cnt_ld, cnt_en, busy;
    output [1:0] state;
    reg [1:0] state, pstate, nstate;
    reg        ld_xi, iterate, cnt_ld, cnt_en, busy;

    // State encoding
    parameter S0=2'b00, S1=2'b01, S2=2'b10, S3=2'b11;

    // Register logic
    always @(posedge clk or posedge reset)
        begin
            if (rst == 1'b1) pstate <= S0;
            else pstate <= nstate;
            state <= pstate;
        end
end
```


Example Architecture – GLITCH

```
// Transition and output logic
always @(pstate or ld_b or done)
    begin
        // Default assignments
        iterate = 1'b0;
        cnt_ld = 1'b0;
        busy = 1'b0;
        cnt_en = 1'b0;
        case (pstate)
            S0: if (ld_b==1'b1) nstate = S1;
                else nstate = S0;
            S1: begin
                    iterate = 1'b1;
                    ld_xi = 1'b1;
                    cnt_ld = 1'b1;
                    busy = 1'b1;
                    nstate = S2;
                end
        end
```

 Example Architecture – GLITCH

```
S2: begin
    cnt_en = 1'b1;
    iterate = 1'b1;
    busy = 1'b1;
    if (done==1'b1) nstate = S3;
    else nstate = S2;
end
S3: begin
    busy = 1'b1;
    nstate = S0;
end
default: nstate = S0;
endcase
end
endmodule
```

Simulation Waveform (GLITCH) *(timing simulation result)*




Example Controller (NO GLITCH)

```
module contrlr1 (state, ld_xi, iterate, cnt_ld,
                cnt_en, busy, ld_b, done, clk, reset);
    input        clk, reset, ld_b, done;
    output       ld_xi, iterate, cnt_ld, cnt_en, busy;
    output [1:0] state;
    reg [1:0]    state, pstate, nstate;
    reg          ld_xi, iterate, cnt_ld, cnt_en, busy;

    // State encoding
    parameter S0=2'b00, S1=2'b01, S2=2'b11, S3=2'b10;


    // Register logic
    always @(posedge clk or posedge reset)
        begin
            if (rst == 1'b1) pstate <= S0;
            else pstate <= nstate;
            state <= pstate;
        end
end
```

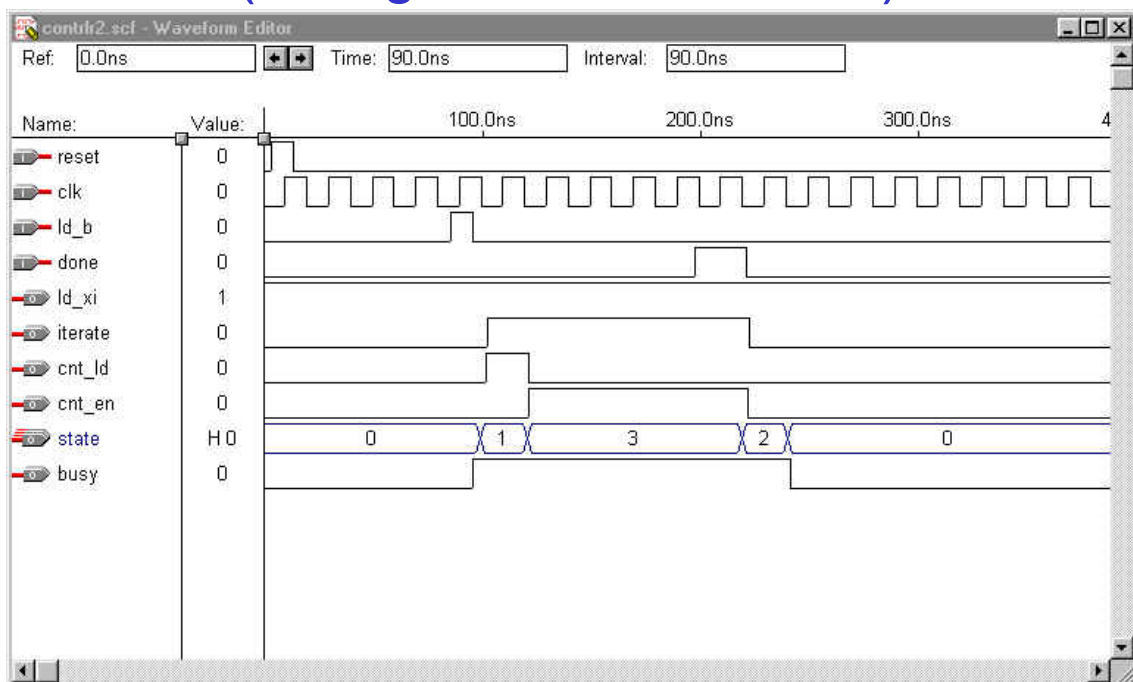Simulation Waveform (NO GLITCH) *(timing simulation result)*




Technology Mapping (GLITCHES)

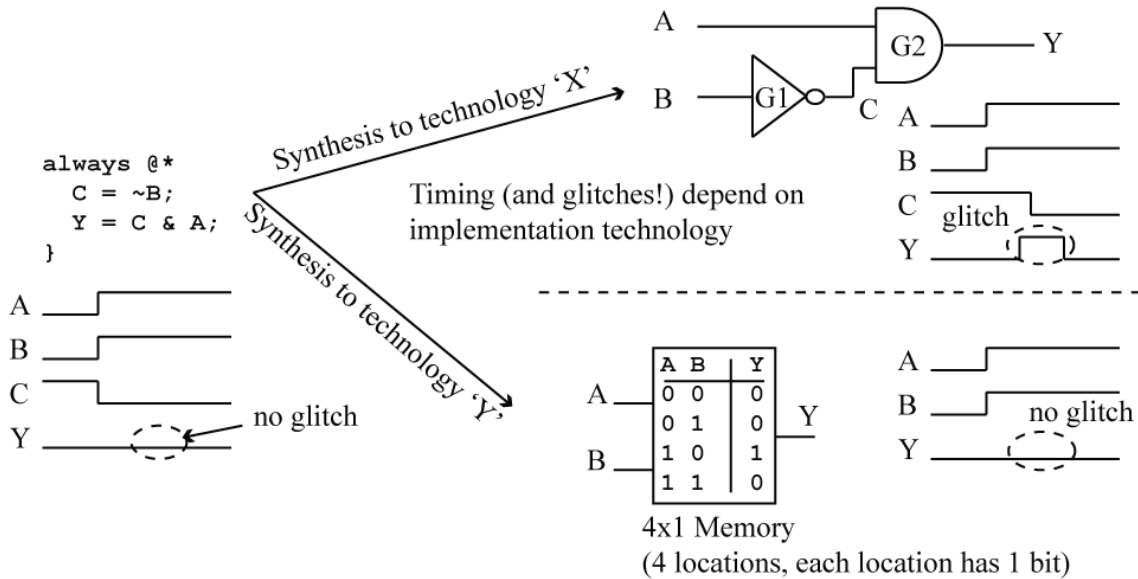Previous Example Mapped to Altera EPM7XXX Device



Minimum Bit-Change State Assignment

 - Previous Example State Diagram Looked Like:




“Glitchy” Encoding:
 s0=00, s1=01, s2=10, s3=11

No “Glitch” Encoding:
 s0=00, s1=01, s2=11, s3=10

*Single bit Change along any transition
 - Gray Code is One way to do it*


Gray Code

 - Used Along Karnaugh Map Edges
 - To Generate:
00 01 11 10 *REFLECTED GRAY CODE*
 - Reverse Sequence:
00 01 11 10 **10 11 01 00**
 - Add Additional 0 to First and 1 to Reversed Sequences:
000 001 011 010 110 111 101 100
- What About?



Minimum-Bit Change Code

 
- Can Assign a “Weight” to Each Transition, W_i
 $W_i = \#$ of bit Changes
- Minimize Sum of Weights
- Gray Code Assumes Equal Weight Transitions
- Not Always Possible



Prioritized Adjacency Strategy

- Assign Adjacent Encodings (differ by 1-bit Only) to:
 1. States With Common Destination
 2. States With Common Source
 3. States With Common Output
- Priority is:
 1. States With Same Next State for a Given Input Value
 2. Destination (next) States With Common Source (present) State
 3. States With Same Output Value for Same Input Values

Prioritized Adjacency Strategy example

 

Priorities

1. (s1, s2) - Both have same NS (s3) with same input (0)
2. (s1,s2) - Both are NS from Common PS (s0)
3. (s0,s1), (s2,s3) - Both have Same Output 0(1) for Same Input 0(0)

Minimum Length Codes


- Smallest Possible Number of Bits per State Vector
 - to represent R states the length must be $k = \lceil \log_2 R \rceil$
- Minimum Length Codes Guarantee Minimal Number of Memory Elements are Used
- N is Number of Possible State Assignments

$$N = \prod_{i=0}^{R-1} \binom{2^k - i}{1} = \prod_{i=0}^{R-1} (2^k - i) = (2^k)! - (2^k - R)!$$

$$\binom{A}{B} = \frac{A!}{(A-B)!B!}$$

State Transition Diagram

Not Simplified!

 

nd/dc – nickel or dime/dispense product and/or change
product cost is 15¢

**M. Clive, Bebop to Boolean Boogie*

Minimum Length Codes-Example

- Vending Machine Example: $R=5$
 - to represent $R=5$ states the length must be $k=\lceil \log_2 5 \rceil=3$

$$\begin{aligned} N &= \prod_{i=0}^{R-1} \binom{2^k - i}{1} = \binom{8}{1} \binom{7}{1} \binom{6}{1} \binom{5}{1} \binom{4}{1} \\ &= \left(\frac{8!}{7!} \right) \left(\frac{7!}{6!} \right) \left(\frac{6!}{5!} \right) \left(\frac{5!}{4!} \right) \left(\frac{4!}{3!} \right) = \left(\frac{8!}{3!} \right) \\ &= 8 \cdot 7 \cdot 6 \cdot 5 \cdot 4 = 56 \cdot 30 \cdot 4 = 56 \cdot 120 = 6720 \end{aligned}$$

Minimum Length State Assignment

- Each Possible Assignment can Require Different Logic
- Register/Memory Element Type Also Affects the Logic
- Analyzing all 6720 Assignments for Example for Minimized SOP 2-Level Logic Yields the Following:

| <i>Number of Solutions</i> | <i>Number of Product Terms</i> |
|----------------------------|--------------------------------|
| 138 | 7 |
| 852 | 8 |
| 1876 | 9 |
| 3094 | 10 |
| 570 | 11 |
| 190 | 12 |

TOTAL: 6720

$$\frac{138}{6720} \cong 2.1\%$$

**M. Clive, Bebop to Boolean Boogie*

Minimum Length State Assignment

- Of the 2.1% that Yield 7 Product Terms
Look at Literal Count

| <i>Number of Solutions</i> | <i>Number of Literals</i> |
|----------------------------|---------------------------|
| 66 | 17 |
| 24 | 18 |
| 48 | 19 |

$$\text{TOTAL: } 138 \quad \frac{66}{6720} \cong 1\%$$

- Given that Minimum Length State Assignment is Required
- Chances of Optimal Assignment if “Randomly” Assign State Vectors is Less Than 1%!!!!

**M. Clive, Bebop to Boolean Boogie*

Optimum State Assignment for Example

- One of the 66 Optimum (in terms of minimized product and literal count) is:

| <i>Symbolic State</i> | <i>State Vector</i> |
|-----------------------|---------------------|
| 0¢ | 100 |
| 5¢ | 101 |
| 10¢ | 000 |
| 15¢ | 001 |
| 20¢ | 011 |

- Brute Force Approach for FPGA Based State Assignment Using Minimum Length Vectors:
 - 1) Choose Device
 - 2) Synthesize For all Possible Encodings
 - 3) Use Analysis tools (timing and area reports)

**M. Clive, Bebop to Boolean Boogie*

State Assignment for Delay Minimization

- Approaches can be Based on Area, Delay, Power Minimization
- “One-hot” is Usual Approach for Speed
 - One Bit in Vector for Each State
 - Only a Single Bit is Set, All Others are Zero-valued
 - Always 2-bit Adjacent State Change
- Can Result in Simple and Fast Transition Logic Networks
- Requires Number of Storage Elements Equal to Number of States
- Usually Not Helpful for Small Number of States in Controller
- Often Used for FPGA Designs Since Operating Speed is Typically Harder Constraint

Example (from Vending Machine Example Earlier)

| <i>Symbolic State</i> | <i>Optimum Min. Length State Vector</i> | <i>1-hot Encoded State Vector</i> |
|-----------------------|---|-----------------------------------|
| 0¢ | 100 | 00001 |
| 5¢ | 101 | 00010 |
| 10¢ | 000 | 00100 |
| 15¢ | 001 | 01000 |
| 20¢ | 011 | 10000 |

There are Still Multiple Choices for a One-hot Encoding!!

State Assignment (Encoding) Summary

- Encoding of FSM states is an implementation decision
- For K states, need a minimum of $\lceil \log_2(K) \rceil$ DFFs
- Minimal encoding examples for two FF Controller:
 - S0 = 00, S1 = 01, S2 = 10 (Binary-counting order)
 - S0 = 00, S1 = 01, S2 = 11, (Gray code for S0->S1->S2)
Gray code usually faster less logic than counting order
 - Gray Code not Always Possible - Try to Use Minimal Adjacent Bit-Change Coding
 - Multiple Minimal Bit-Change Encodings Possible
 - Can Consider Which State Transitions Occur Most Frequently for Minimal Bit-change Encoding Assignment

State Assignment (Encoding) Summary

- One-hot encoding, one FF per state
 - S0 = 001, S1 = 010, S2 = 100
 - For large FSMs (in terms of states), one-hot can be faster than minimal adjacent bit-change encoding
 - One-hot Still has Many Different State Assignments
- Optimal Assignment is an NP-hard Problem
 - Good heuristic Methods have been Developed
 - Public Domain Programs KISS, NOVA, MUSTANG, JEDI
 - Different Methods for Different Criteria: Area, Delay, Power
 - Different Methods for Different Implementation Technology: PLDs, FPGAs, Custom
- Symbolic Encoding Support
 - New Generation HDLs Support User-defined Types (`#define`) Such as SystemVerilog and SystemC
 - Some Synthesis Tools Incorporate Automated State Assignment (Quartus does not have this Feature)