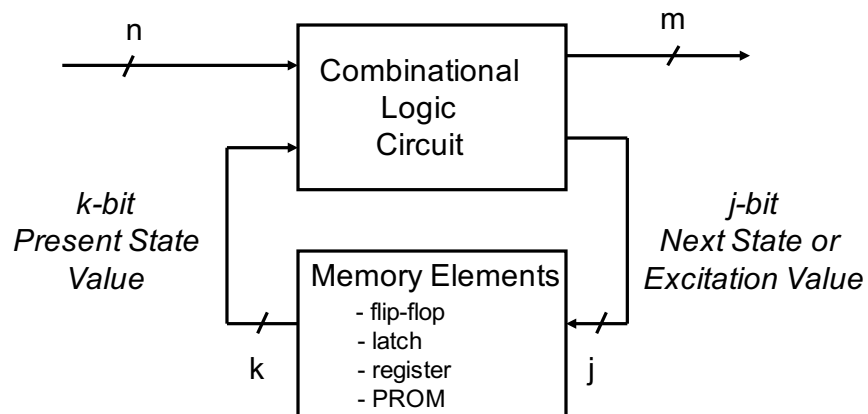


Sequential Systems Review

- Combinational Network
 - Output value only depends on input value
- Sequential Network
 - Output Value depends on input value and **present state** value
 - Sequential network must have some way of retaining **state** via memory devices.
 - can be **synchronous** or **asynchronous**
- Synchronous Sequential Network
 - Use a clock signal in a **synchronous** sequential system to control changes between states

1


Sequential System Diagram



- m outputs only depend on k PS bits - Moore Machine
 - *REMEMBER: Moore is Less !!*
- m outputs depend on k PS bits AND n inputs - Mealy Machine


2

Controller Block Diagrams

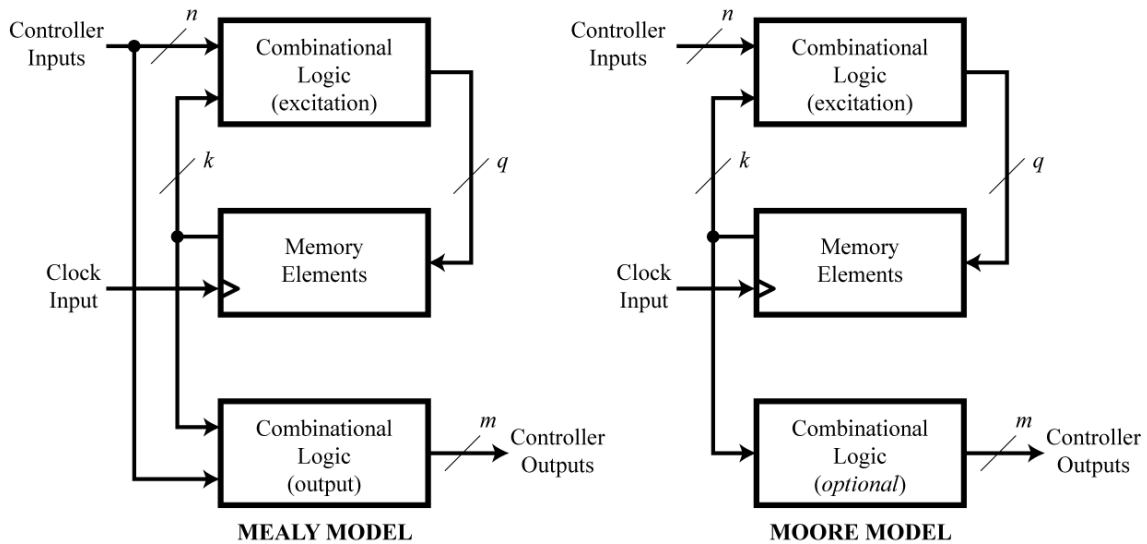

3

Clock Signal

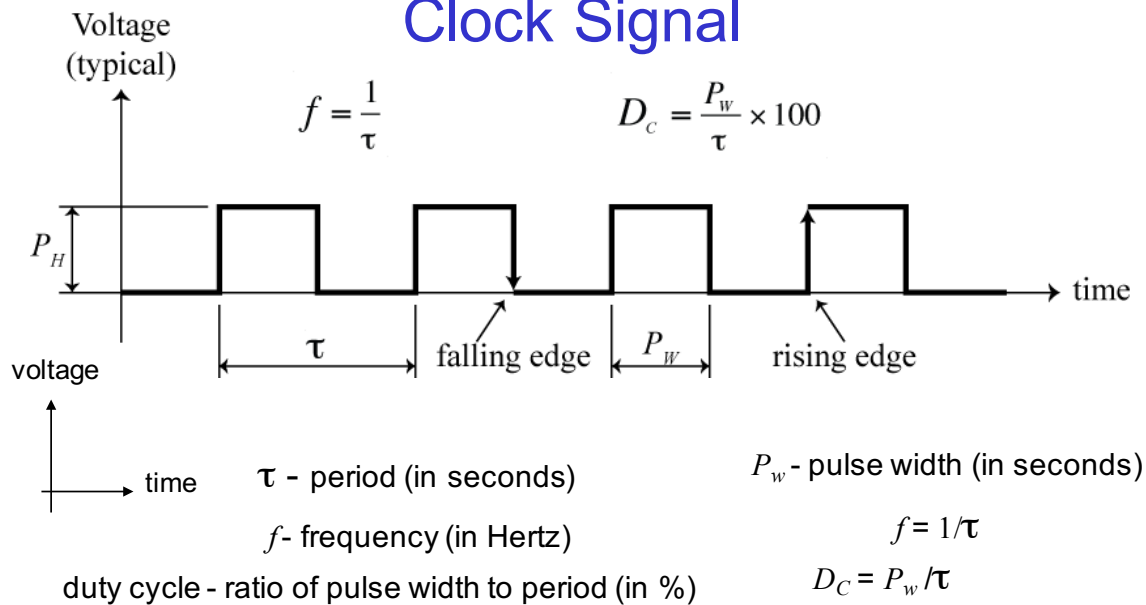

millisecond (ms) 10^{-3}	Kilohertz (kHz) 10^3
microsecond (μ s) 10^{-6}	Megahertz (MHz) 10^6
nanosecond (ns) 10^{-9}	Gigahertz (GHz) 10^9

4

Clock Signal Example

What is the pulse-width of a 4.77 MHz clock with a 30% duty cycle?

5

Clock Signal Example

What is the pulse-width of a 4.77 MHz clock with a 30% duty cycle?

$$\tau = 1/f = (4.77 \times 10^6)^{-1} = 2.096 \times 10^{-7} = 210 \text{ ns}$$

6

Clock Signal Example

What is the pulse-width of a 4.77 MHz clock with a 30% duty cycle?


$$\tau = 1/f = (4.77 \times 10^6)^{-1} = 2.096 \times 10^{-7} = 210 \text{ ns}$$

$$P_w = (\text{duty cycle}) \times \tau = (0.3) \times (210 \text{ ns}) = 63 \text{ ns}$$


7

Storage Elements

 (a) level-sensitive storage element
(D-latch)




latch is transparent to changes on d

 


q follows d when g is high

 (b) edge-triggered storage element
(data flip-flop, or DFF)




capture the d input

 

q follows d on rising edge of clk


8

D FF, D Latch operation

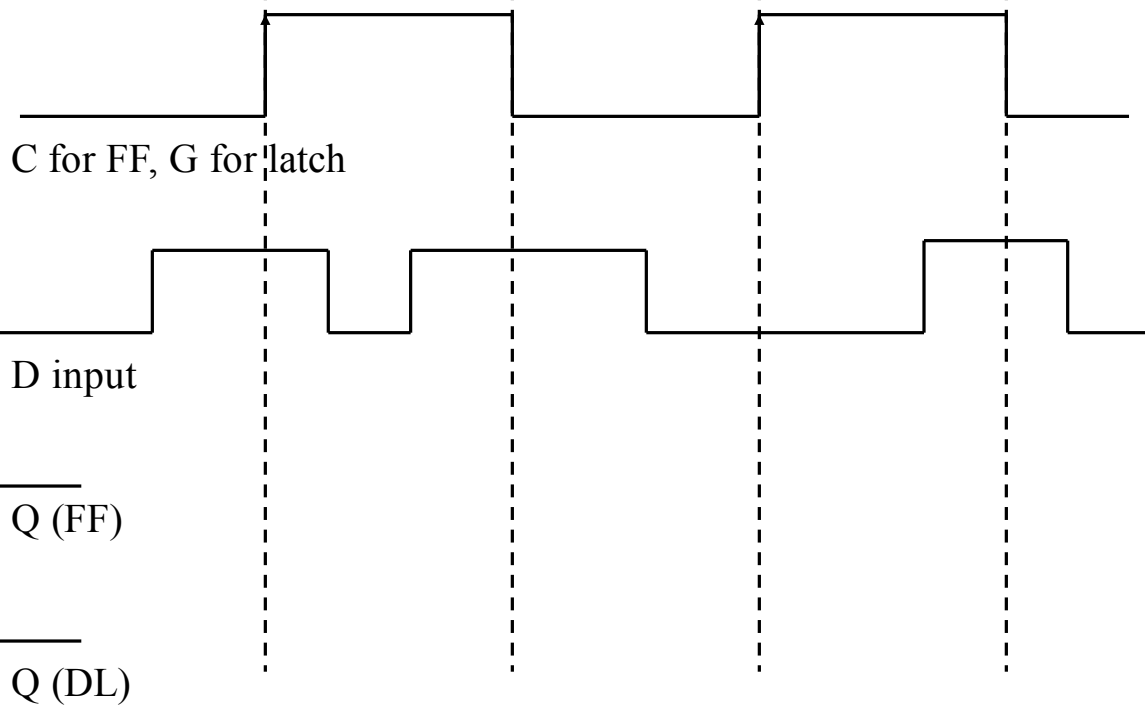


9

D FF, D Latch operation

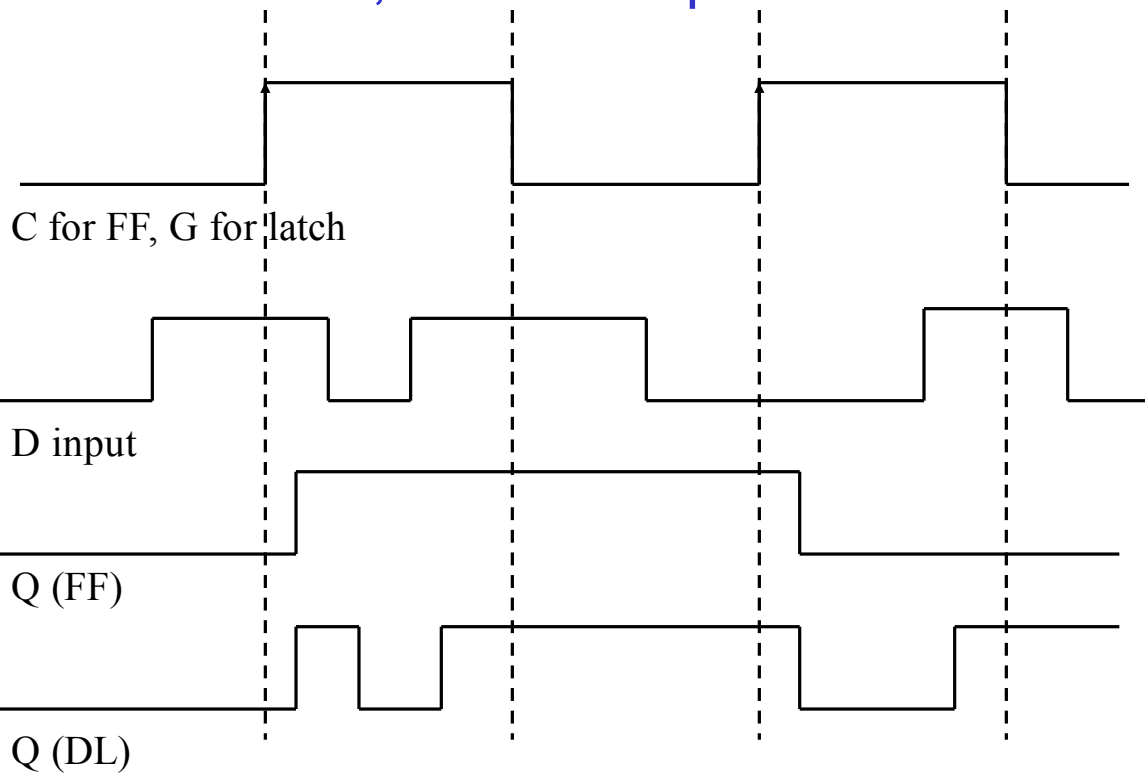

10


Other State Elements

 

J	K	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	Q'(t)

JK can be useful for single bit flags with separate set(J), reset(K) control.

RARELY USED

 

T	Q(t+1)
0	Q(t)
1	Q'(t)

Can be useful for asynchronous counter design.

RARELY USED

11


DFFs are most common

- Most FPGA families only have DFFs
- DFF is fastest, simplest (fewest transistors) of FFs
- Other FF types (T, JK) can be built from DFFs
- We will use DFFs almost exclusively in this class
 - Will always use edge-triggered state elements (FFs), not level sensitive elements (latches).

12

Synchronous vs Asynchronous Inputs

 Synchronous input: Output will change after active clock edge
Asynchronous input: Output changes independent of clock




State elements often have async set, reset control.

D input is synchronous with respect to Clk

S, R are asynchronous. Q output affected by S, R independent of C. Async inputs are dominant over Clk.

13


D FF with async control

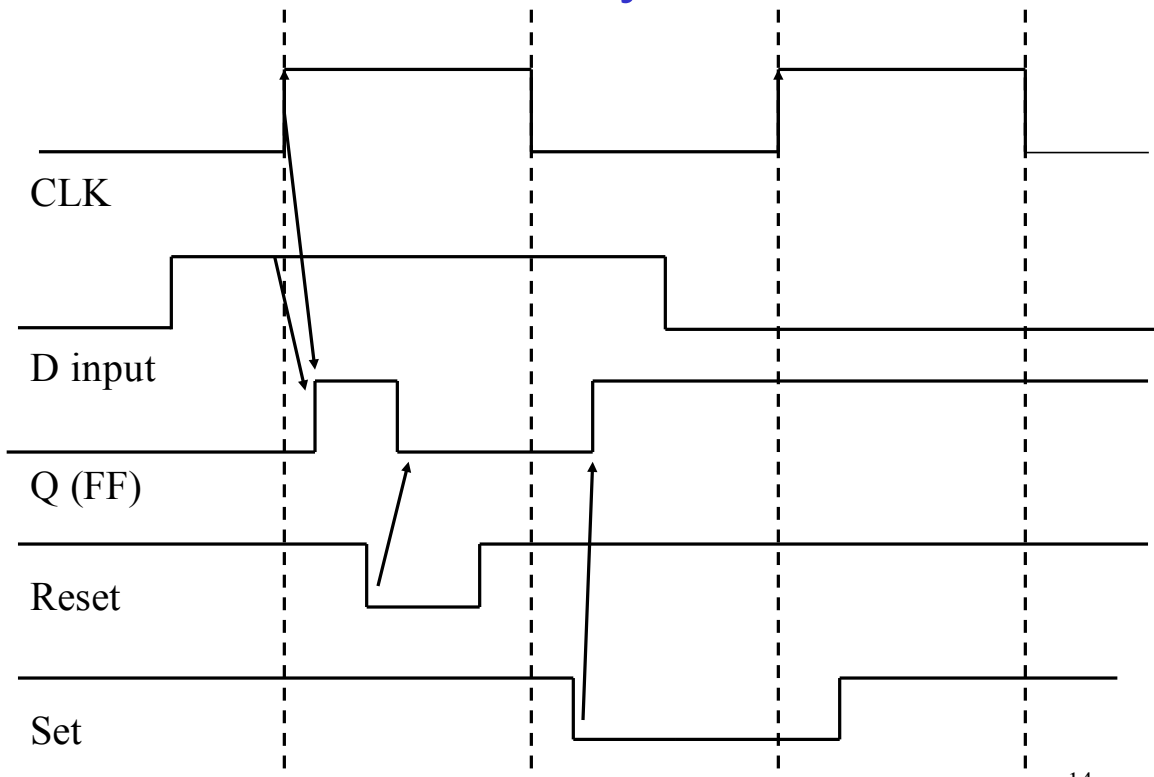

14

D-Flip-Flop with Async. Set/Res

(a) DFF with asynchronous Set/Reset

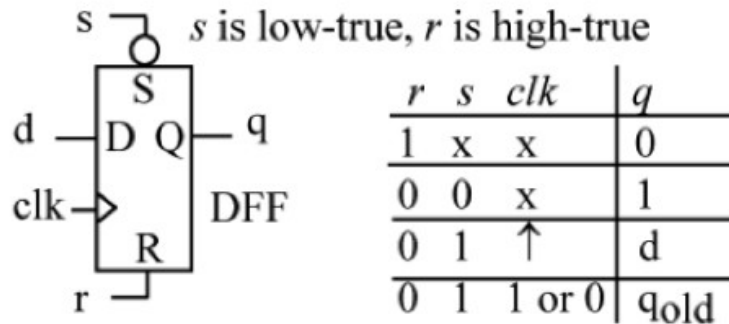


```
always @(posedge clk or
        posedge r or
        negedge s)
```

```
begin
    if (r) q <= 1'b0;
    else if (!s) q <= 1'b1;
    else q <= d;
end
```

15

D-Flip-Flop with Async. Set/Res

 


1. d input is captured on rising clock edge as r, s are negated; q becomes '1'.
2. r input is asserted; q becomes '0'.
3. s input is asserted; q becomes '1'.
4. assertion of s input (a) overrides clock input (b), so q output remains as '1'.

16

D-Flip-Flop with Sync. Set/Res


(b) DFF with synchronous preset/clear

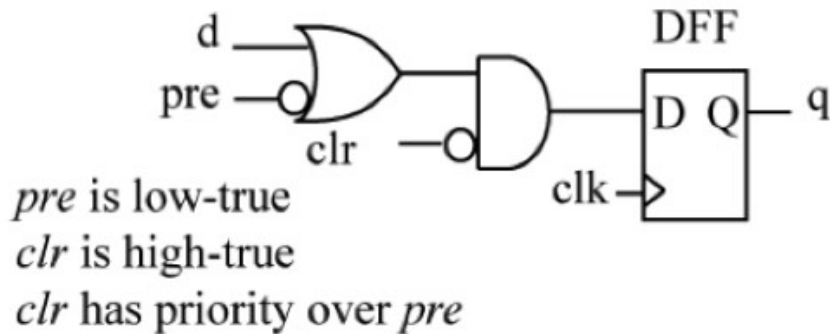

```
always @(posedge clk)
begin
    q <= d; //lowest priority
    if (!pre) q <= 1'b1;
    if (clr) q <= 1'b0; //highest priority
end
```

17

D-Flip-Flop with Sync. Set/Res

 

1. *d* input is captured on rising clock edge as *clr*, *pre* are negated; *q* becomes '1'.
2. assertion of synchronous input has no effect if does not occur on the active clock edge
3. *clr* input is asserted on rising clock edge; *q* becomes '0'.
4. *pre* input is asserted on rising clock edge; *q* becomes '1'.

18

FF Timing

- Propagation Delay
 - C2Q: Q will change some propagation delay after change in C. Value of Q is based on D input for DFF.
 - S2Q, R2Q: Q will change some propagation delay after change on S input, R input
 - Note that there is NO propagation delay D2Q for DFF!
 - D is a Synchronous INPUT, no prop delay value for synchronous inputs


19

Setup, Hold Times

- Synchronous inputs (e.g. D) have Setup, Hold time specification with respect to the CLOCK input
- Setup Time: the amount of time the synchronous input (D) must be *stable before* the active edge of clock
- Hold Time: the amount of time the synchronous input (D) must be *stable after* the active edge of clock.

20

Setup, Hold Time

 

If changes on D input violate either setup or hold time, then correct FF operation is not guaranteed.

Setup/Hold measured around active clock edge.