

Majority Gate with Temporary Signals

The following version of the majority gate uses some temporary “wires”

```
// Majority Logic Circuit
module maj_circ(Y, A, B, C);
    input A, B, C;
    output Y;
    wire x1, x2, x3; //Optional
    assign x1 = A&B;
    assign x2 = A&C;
    assign x3 = B&C;
    assign Y = x1|x2|x3;
endmodule
```

1

Concurrent Assignment with Ternary Select

```
assign mux_out = (select==1'b0) ? q0 : q1;
```

`if` statement is procedural (sequential)

Used inside `begin – end` Block

Similar to `if` Statement but Concurrent Version

2

Majority Gate with conditional statement

The following version of the majority gate uses a conditional concurrent statement:

```
// Majority Logic Circuit
module maj_circ(Y, A, B, C);
    input A, B, C;
    output Y;
    assign Y = ((A&&B) || (A&&C) || (B&&C))
               ? 1'b1 : 1'b0;
endmodule
```

You will find that there are many different ways to accomplish the same result in Verilog. There is usually no best way; just use one that you feel most comfortable with.

Concurrent Versus Sequential Statements

- The statements we have looked at so far are called **concurrent** statements.
 - Each concurrent statement will synthesize to a block of logic.
- Another class of Verilog statements are called **procedural (sequential)** statements.
 - Sequential statements can ONLY appear inside of a **always** or an **initial** block.
 - An **always** block is considered to be a single concurrent statement
 - Can have multiple **always** blocks in a module
 - Usually use **always** blocks to describe complex combinational or sequential logic

Comments on always block model

- always statement executes at every simulator time cycle

```
always CLK = ~CLK; //Will Loop indefinitely
```

- General Form:

```
always [timing_control]procedural statement(s)
```

- always statement with delay control

```
always #5 CLK = ~CLK; //Waveform CLK is 10 time units
```

- always statement with event control

```
CL always @(A or B or C) //Event on A, B, or C
```

```
CL always @(CLK) //Event on rising-falling edge of CLK
```

```
Sto always @(posedge CLK) //Event on rising edge of CLK
```

```
Sto always @(negedge CLK) //Event on falling edge of CLK
```

5

Verilog Always Block

(a) Combinational always block using an if statement.

```
module mux2to1(s,a,b,y);
input s,a,b;
output y;

reg y;

//use an if statement
always @(a or b or s)
begin
if (s) y = b;
else y = a;
end

endmodule
```

(b) Combinational always block using Boolean operations.

```
module mux2to1(s,a,b,y);
input s,a,b;
output y;

reg y;

//use boolean ops
always @(a or b or s)
begin
y = (b & s) | (a & ~s);
end

endmodule
```

(c) Combinational always block using Boolean operations and intermediate values.

```
module mux2to1(s,a,b,y);
input s,a,b;
output y;

reg y, na, nb;

//use intermediates
//and implicit event
//list
always @*
begin
nb = b & s;
na = a & ~s;
y = na | nb;
end

endmodule
```


6

Precedence in Always Block

(a) `clr` takes precedence over `ld` if both are '1'

```
always @(ld or clr or d or q_old)
begin
  q = q_old;
  if (ld) q = d;
  if (clr) q = 0;
end
```


ld	clr	q
0	0	q_old
0	1	0
1	0	d
1	1	0

 

(b) `ld` takes precedence over `clr` if both are '1'

```
always @(ld or clr or d or q_old)
begin
  q = q_old;
  if (clr) q = 0;
  if (ld) q = d;
end
```

ld	clr	q
0	0	q_old
0	1	0
1	0	d
1	1	d

 

7

Majority Gate using *always* block and *if* statement

```
// Majority Logic Circuit
module maj_circ(Y, A, B, C);
  input A, B, C;
  output Y;
  reg Y;
  always @(A or B or C)
  begin
    if ((A==1'b1) && (B==1'b1))
      Y = 1'b1;
    else if ((A==1'b1) && (C==1'b1))
      Y = 1'b1;
    else if ((B==1'b1) && (C==1'b1))
      Y = 1'b1;
    else
      Y = 1'b0;
  end
endmodule
```

8

Use of *if-else*

```
// Majority Logic Circuit
module maj_circ(Y, A, B, C);
  input A, B, C;
  output Y;
  reg Y;
  always @(A or B or C)
    if((A&&B) ||
        (A&&C) ||
        (B&&C))
      Y = 1'b1;
    else
      Y = 1'b0;
endmodule
```

Comments:

Module name is maj_circ

Used an 'else' clause to specify what the output should be if the if condition test was not true.

CAREFUL! Instead of Remembering Boolean Operator Precedence, Just Use Parentheses to Make Sure

9

Unassigned outputs in Always blocks

A common mistake in writing a combinational module is to leave an output unassigned. If there is a path through the block in which an output is NOT assigned a value, then that value is unassigned.

```
// Majority Logic Circuit
module bad_maj_circ(Y, A, B, C);
  input A, B, C;
  output Y;
  reg Y;
  always @(A or B or C)
    if((A&&B) ||
        (A&&C) ||
        (B&&C))
      Y = 1'b1;
endmodule
```

What is missing here?

10

Unassigned outputs in Always blocks

A common mistake in writing a combinational module is to leave an output unassigned. If there is a path through the block in which an output is NOT assigned a value, then that value is unassigned.

```
// Majority Logic Circuit
module bad_maj_circ(Y, A, B, C);
  input A, B, C;
  output Y;
  reg Y;
  always @(A or B or C)
    if((A&&B) ||
        (A&&C) ||
        (B&&C))
      Y = 1'b1;
endmodule
```

What if $((A \& B) | (A \& C) | (B \& C))$ equals $1'b0$?₁


Comments on Previous Example

- In the previous `always` block, the `ELSE` clause was left out. If the `'if'` statement condition is false, then the output `Y` is not assigned a value.
 - In synthesis terms, this means the output `Y` should have a **LATCH** placed on it! (*INFERRED LATCH*)
 - The synthesized logic will have a latch placed on the `Y` output; once `Y` goes to a `1'b1`, it can NEVER return to a `1'b0`!!!!
- This is probably *the #1 student mistake* in writing `always` blocks. To avoid this problem do one of the following things:
 - ALL signal outputs of the `always` block should have **DEFAULT** assignments.
 - OR, all `'if'` statements that affect a signal must have `ELSE` clauses that assign the signal a value if the `'if'` test is false.


Inferred Latch

2:1 Multiplexer Example

 (a) Incorrect, produces an inferred latch as no assignment is made to q if ld is '0'



 (b) Correct, produces combinational logic



13

Priority circuit example

```

module pri_dec(dout,y7,y6,y5,y4,y3,y2,y1);
  input y7,y6,y5,y4,y3,y2,y1;
  output [2:0] dout;
  reg [2:0] dout;
  always @(y7 or y6 or y5 or y4 or y3
           or y2 or y1)
  begin
    if (y7==1'b1) dout = 3'b111;
    else if (y6 == 1'b1) dout = 3'b110;
    else if (y5 == 1'b1) dout = 3'b101;
    else if (y4 == 1'b1) dout = 3'b100;
    else if (y3 == 1'b1) dout = 3'b011;
    else if (y2 == 1'b1) dout = 3'b010;
    else if (y1 == 1'b1) dout = 3'b001;
    else dout = 3'b000;
  end
endmodule
  
```

This priority circuit has 7 inputs;
Y7 is highest priority, Y1 is lowest priority.

Three bit output should indicate the highest priority input that is a '1' (ie. if Y6 = '1', Y4 = '1', then output should be "110"). If no input is asserted, output should be "000".

14

Comments on Priority Example

- The `dout` signal is a 3 bit output bus.
 - `reg [2:0] dout` describes a 3 bit bus where `dout[2]` is most significant bit, `dout[0]` is least significant bit.
 - `reg [0:2] dout` is also a 3 bit bus, but `dout[0]` is MSB, `dout[2]` is LSB. **NOT RECOMMENDED!**
- A bus assignment can be done in many ways:
 - `dout = 3'b110;` assigns all three bits
 - `dout[2] = 1'b1;` assigns only bit #2
 - `dout[1:0] = 2'b10;` assigns two bits of the bus.
- This module used the `else if` form of the `if` statement
 - This is called an `else if` chain.

15

Priority Circuit with just IF statements

```
module pri_dec(dout,y7,y6,y5,y4,y3,y2,y1);
  input y7,y6,y5,y4,y3,y2,y1;
  output [2:0] dout;
  reg [2:0] dout;
  always @(y7 or y6 or y5 or y4 or y3
          or y2 or y1)
  begin
    dout = 3'b000;
    if (y1==1'b1) dout = 3'b001;
    if (y2==1'b1) dout = 3'b010;
    if (y3==1'b1) dout = 3'b011;
    if (y4==1'b1) dout = 3'b100;
    if (y5==1'b1) dout = 3'b101;
    if (y6==1'b1) dout = 3'b110;
    if (y7==1'b1) dout = 3'b111;
  end
endmodule
```

By reversing the order of the assignments, we can accomplish the same as the `else if` priority chain.

In an `always` block, the LAST assignment to the output is what counts.

16

An attempt at a Priority Circuit

```
module pri_dec (dout,y7,y6,y5,y4,y3,y2,y1);
  input y7,y6,y5,y4,y3,y2,y1;
  output [2:0] dout;
    assign dout = (y1==1'b1) ? 3'b001 : 3'b000;
    assign dout = (y2==1'b1) ? 3'b010 : 3'b000;
    assign dout = (y3==1'b1) ? 3'b011 : 3'b000;
    assign dout = (y4==1'b1) ? 3'b100 : 3'b000;
    assign dout = (y5==1'b1) ? 3'b101 : 3'b000;
    assign dout = (y6==1'b1) ? 3'b110 : 3'b000;
    assign dout = (y7==1'b1) ? 3'b111 : 3'b000;
endmodule
```

Is anything wrong here?

17

Another attempt at a Priority Circuit (same as before-diff. syntax)

```
module pri_dec (dout,y7,y6,y5,y4,y3,y2,y1);
  input y7,y6,y5,y4,y3,y2,y1;
  output [2:0] dout;
    assign dout = (y1==1'b1) ? 3'b001 : 3'b000,
      dout = (y2==1'b1) ? 3'b010 : 3'b000,
      dout = (y3==1'b1) ? 3'b011 : 3'b000,
      dout = (y4==1'b1) ? 3'b100 : 3'b000,
      dout = (y5==1'b1) ? 3'b101 : 3'b000,
      dout = (y6==1'b1) ? 3'b110 : 3'b000,
      dout = (y7==1'b1) ? 3'b111 : 3'b000;
endmodule
```

Is anything wrong here?

18

Comments on “bad” Priority Circuits

- Bad Attempts for Priority Circuit
- Problems in this Description
 - Multiple Concurrent Statements Driving `dout` Signal
 - Causes Multiple Gate Outputs to be Tied Together
 - Creates Unknown Logic Condition on Bus
- Writer seems to think that the order of the concurrent statements makes a difference
 - The order in which you arrange concurrent statements **MAKES NO DIFFERENCE**. The synthesized logic will be the same.
 - Ordering of statements only makes a difference within an `always(initial)` block. This is why statements within such blocks are called 'sequential' statements; the logic synthesized reflects the statement ordering (only for assignments to the same output).

19

Priority Circuit with Concurrent Statement

No procedural (sequential) block; just one concurrent statement.

```
module pri_dec (dout,y7,y6,y5,y4,y3,y2,y1);
  input y7,y6,y5,y4,y3,y2,y1;
  output [2:0] dout;
  assign dout = (y1==1'b1) ? 3'b001 :
    ((y2==1'b1) ? 3'b010 :
    ((y3==1'b1) ? 3'b011 :
    ((y4==1'b1) ? 3'b100 :
    ((y5==1'b1) ? 3'b101 :
    ((y6==1'b1) ? 3'b110 :
    ((y7==1'b1) ? 3'b111 : 3'b000)))));
endmodule
```

20

4-to-1 mux with 8 bit Datapaths

```
module mux8 (dout,A,B,C,D,SEL) ;
    input [7:0] A,B,C,D;
    input [1:0] SEL;
    output [7:0] dout;
    assign dout = (SEL==2'b00) ? A :
                  ((SEL==2'b01) ? B :
                   ((SEL==2'b10) ? C :
                    ((SEL==2'b11) ? D : 8'hxx)));
endmodule
```

21

Comments on MUX example

- This is one way to write a mux, but it is not the best way. The nested ternary assignment statement is actually a ***priority*** structure.
 - A ***mux has no priority*** between inputs, just a simple selection.
 - The synthesis tool has to work harder than necessary to understand that all possible choices for **SEL** are specified and that no priority is necessary.
- Just want a simple selection mechanism.

22

Multiplexers in Verilog

(a) Four-bit 4-to-1 mux using if-else chain

```
module mux4to1_4bit(s,a,b,c,d,y);
input  [1:0] s;
input  [3:0] a,b,c,d;
output [3:0] y;

reg [3:0] y;

always @*
begin
    if (s == 2'b00) y = a;
    else if (s == 2'b01) y = b;
    else if (s == 2'b10) y = c;
    else y = d;
end
endmodule
```

2-bit binary constant

equality operator

Priority Structure

(b) Four-bit 4-to-1 mux using a case statement chain

```
module mux4to1_4bit(s,a,b,c,d,y);
input  [1:0] s;
input  [3:0] a,b,c,d;
output [3:0] y;

reg [3:0] y;

always @*
begin
    case (s)
        2'b00 : y = a;
        2'b01 : y = b;
        2'b10 : y = c;
        default: y = d;
    endcase
end
endmodule
```

Non-Priority Structure

23

Another 4-to-1 Mux using always Block

```
module mux8 (dout,A,B,C,D,SEL);
input [7:0] A, B, C, D;
input [1:0] SEL;
output [7:0] dout;
reg [7:0]dout;
always @(SEL or A or B or C or D)
begin
    case (SEL)
        2'b00: dout=A;
        2'b01: dout=B;
        2'b10: dout=C;
        2'b11: dout=D;
        default: dout=8'hxx;
    endcase
end
endmodule
```

This is a **concurrent always block**; the **sequential** statement within the always block is the case statement.



24

Full and Ripple Adders



A	B	Ci	S	Co
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Truth Table for Full Adder
 Ci - Carry In
 S - Sum
 Co - Carry Out
  
$$Co = \text{Majority}(A, B, Ci) = (A \wedge B) \vee (A \wedge Ci) \vee (B \wedge Ci)$$



 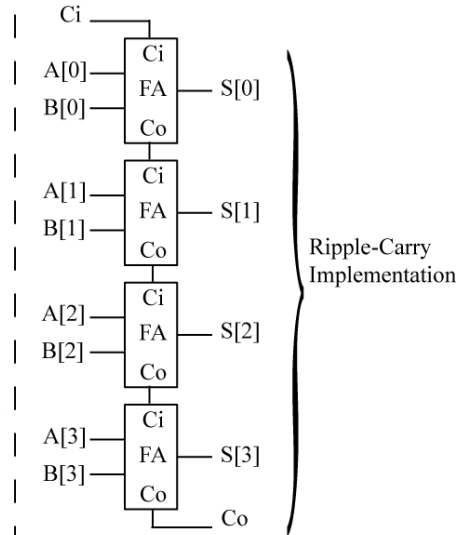(a) Full Adder Truth table, Boolean equations, Symbol



(b) 4-bit adder symbol and Ripple Carry Implementation

Adders in Verilog

(a) Four-bit adder with no carry-in or carry-out

```
//4-bit adder
// no carry-in, carry-out
module add4bit ( a, b, s);

input [3:0] a,b;
output [3:0] s;

assign s = a + b;

endmodule
```

(b) Four-bit adder with carry-in, carry-out


```
//4-bit adder with carry-in, carry-out
module add4bit (ci, a, b, s, co);

input ci;
input [3:0] a,b;
output [3:0] s;
output co;

wire [4:0] y;

//do 5-bit sum so that we
// have access to carry out
assign y = {1'b0,a} + {1'b0,b} + {4'b0,ci};
assign s = y[3:0]; //four-bit output
assign co = y[4]; //carry-out


endmodule
```

 

{ } is the concatenation operator

Verilog Synthesis Results

 Even though these two implementations are functionally equivalent, some synthesis tools may produce a slightly more efficient implementation for (b) than (a).




(a)

```
//adder/subtractor
module addsub4bit(sub,a,b,y);

input sub;
input [3:0] a,b;
output [3:0] y;
//          sub=1  sub=0
assign y = sub ?(a-b):(a+b);

endmodule
```

 

(b)

```
//adder/subtractor
module addsub4bit ( sub, a, b, y);

input sub;
input [3:0] a,b;
output [3:0] y;


wire [3:0] btmp;
//          sub=1  sub=0
assign btmp = sub ? ~b : b;
assign y = a + btmp + {3'b0,sub};

endmodule
```

Fixed-Point Multipliers

multiplicand	r_2	r_1	r_0	Binary	Decimal		
multiplier	X s_2	s_1	s_0	1 1 1	7		
partial product	$s_0 * r_2$	$s_0 * r_1$	$s_0 * r_0$	X <u>1 0 1</u>	X <u>5</u>		
	$s_1 * r_2$	$s_1 * r_1$	$s_1 * r_0$	1 1 1	35		
	$s_2 * r_2$	$s_2 * r_1$	$s_2 * r_0$	0 0 0			
+	<u>$s_2 * r_2$</u>	<u>$s_2 * r_1$</u>	<u>$s_2 * r_0$</u>	+ <u>1 1 1</u>			
P_5	P_4	P_3	P_2	P_1	P_0	product	<u>1 0 0 0 1 1 = 35</u>

Array Multiplier Structure

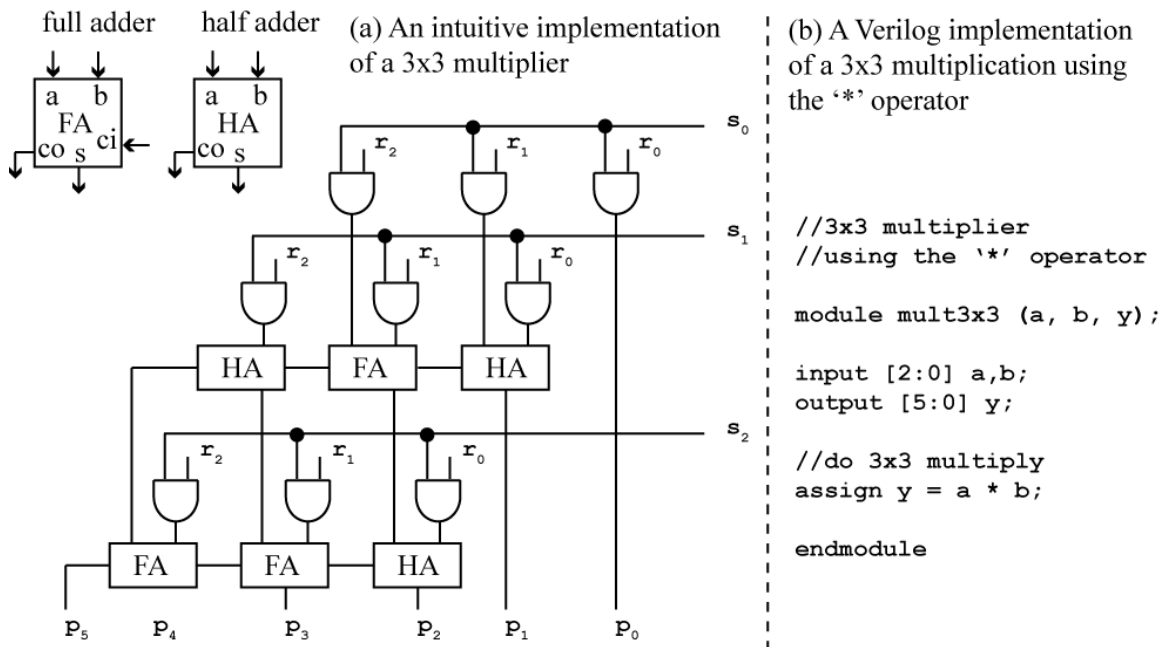

29

Bit Shifting in Verilog

Concatenation Operation

$$\left. \begin{array}{l} a_7 \ a_6 \ a_5 \ a_4 \ a_3 \ a_2 \ a_1 \ a_0 \\ \downarrow \downarrow \downarrow \downarrow \downarrow \downarrow \downarrow \downarrow \\ s_i \ a_7 \ a_6 \ a_5 \ a_4 \ a_3 \ a_2 \ a_1 \\ y_7 \ y_6 \ y_5 \ y_4 \ y_3 \ y_2 \ y_1 \ y_0 \end{array} \right\} \text{(a) right shift}$$

$$y = \{s_i, a[7:1]\}; \quad s_i \text{ is shift input bit}$$


$$\left. \begin{array}{l} a_7 \ a_6 \ a_5 \ a_4 \ a_3 \ a_2 \ a_1 \ a_0 \\ \downarrow \downarrow \downarrow \downarrow \downarrow \downarrow \downarrow \downarrow \\ a_6 \ a_5 \ a_4 \ a_3 \ a_2 \ a_1 \ a_0 \ s_i \\ y_7 \ y_6 \ y_5 \ y_4 \ y_3 \ y_2 \ y_1 \ y_0 \end{array} \right\} \text{(b) left shift}$$

$$y = \{a[6:0], s_i\}; \quad s_i \text{ is shift input bit}$$

30

Bit Shifting with Multiplexers

(a) left/right shift with a multiplexer

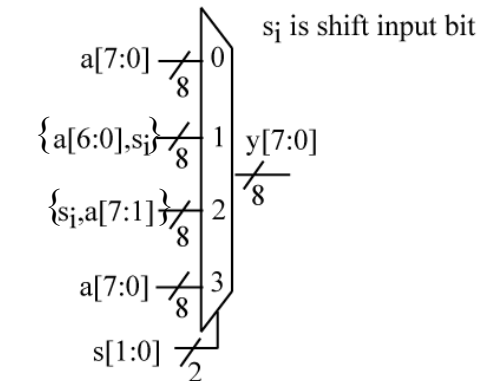

s[0]= sleft (shift left)
s[1]= sright (shift right)

s	y
00	y = a
01	y is a shifted to left
10	y is a shifted to right
11	y = a

(b) Verilog left/right shift

```

module lrshift_8bit (si,sleft,sright,a,y);
    input si,sleft,sright;
    input [7:0] a;
    output [7:0] y;

    reg [7:0] y;
    wire [1:0] s;


    assign s[0] = sleft;
    assign s[1] = sright;

    always @(s or a) begin
        case (s)
            2'b01 : y = {a[6:0],si}; //left shift
            2'b10 : y = {si,a[7:1]}; //right shift
            default: y = a;
        endcase
    end

endmodule
    
```

Multiplexer-based Barrel Shifter

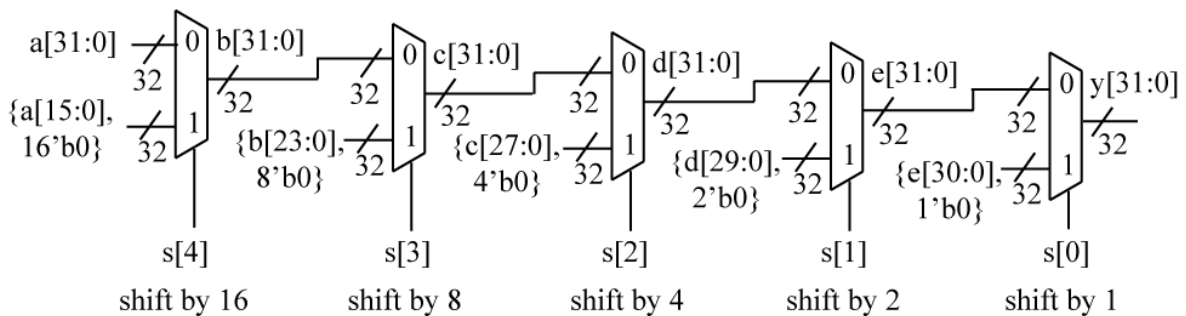(a) Multiplexer implementation of a 32-bit left-shift barrel shifter



(b) Verilog implementation

```

module bshift_32bit (s, a, y);
    input [4:0] s;
    input [31:0] a;
    output [31:0] y;


    assign y = a << s;

endmodule
    
```



Tri-state Buffers



 
 
(a) Tri-state buffer with high-true enable



(high impedance)




(b) Half-duplex communication

  

(c) Bus multiplexing

Bus Multiplexing

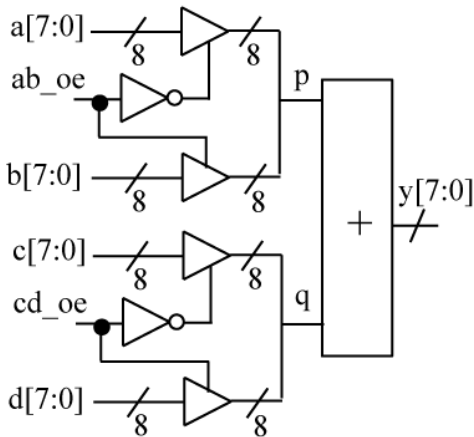(a) Bus multiplexing with tri-state drivers



(b) Verilog implementation

```
//tri-state buffer test
module tsb (a, b, c, d, ab_oe, cd_oe, y);
    input ab_oe, cd_oe;
    input [7:0] a, b, c, d;
    output [7:0] y;
    wire [7:0] p, q;
    //          ab_oe=1 ab_oe=0
    assign p = ~ab_oe ? a : 8'bzzzzzzzz;
    assign p = ab_oe ? b : 8'bzzzzzzzz;
    //          cd_oe=1 cd_oe=0
    assign q = ~cd_oe ? c : 8'bzzzzzzzz;
    assign q = cd_oe ? d : 8'bzzzzzzzz;
    assign y = p + q;
endmodule
```

Assignments to the same wire allowed because of tri-state drivers

Delay Modeling-Simulation

- Timescale Directive
 - ``timescale 1ns/100ps`
 - First number is unit of measurement for delays
 - Second number is precision (round-off increments)
- We will use Default Increments
 - `#` Directive for Delay Modeling
 - Timing Allows for More Accurate Modeling
 - Concept of Back Annotation
- Used ONLY FOR SIMULATION
 - Not Used for Synthesis
 - Back-annotation

35

Verilog Example with Delay

```
// Description of circuit with delay
module circuit_with_delay (A,B,C,x,y);
    input  A,B,C;
    output x,y;
    wire  e;
    and   #(30) g1(e,A,B);
    not   #(10) g2(y,C);
    or    #(20) g3(x,e,y);
endmodule
```

Where does this
come from?



	Time Units (ns)	Input ABC	Output y e x
Initial	-	000	1 0 1
Change	-	111	1 0 1
	10	111	0 0 1
	20	111	0 0 1
	30	111	0 1 0
	40	111	0 1 0
	50	111	0 1 1

36

Verilog Example with Delay

```
// Description of circuit with delay
module circuit_with_delay (A,B,C,x,y);
    input  A,B,C;
    output x,y;
    wire e;
    and  #(30) g1(e,A,B);
    not  #(10) g2(y,C);
    or   #(20) g3(x,e,y);
endmodule
```

t=0:

events: A:0/1 B:0/1 C:0/1


simulations: g1(AND) A=1,B=1,t=30(30)
 g2(NOT) C=1,t=10(10)

© 2002 Prentice Hall, Inc.
 M. Morris Mano
 DIGITAL DESIGN, 3e.

Simulation Scheduled at 10 Simulation Scheduled at 30

Verilog Example (Waveform)
 
```
// Description of circuit with delay
module circuit_with_delay (A,B,C,x,y);
    input  A,B,C;
    output x,y;
    wire e;
    and  #(30) g1(e,A,B);
    not  #(10) g2(y,C);
    or   #(20) g3(x,e,y);
endmodule
```



© 2002 Prentice Hall, Inc.
 M. Morris Mano
 DIGITAL DESIGN, 3e.

Verilog Example with Delay

```
// Description of circuit with delay
module circuit_with_delay (A,B,C,x,y);
    input  A,B,C;
    output x,y;
    wire e;
    and  #(30) g1(e,A,B);
    not  #(10) g2(y,C);
    or   #(20) g3(x,e,y);
endmodule
```

t=10:


events: y:1/0

simulations: g3(OR) e=0,y=0,t=20(30)

Another Simulation Scheduled at 30 ³⁹

Verilog Example (Waveform)
 
```
// Description of circuit with delay
module circuit_with_delay (A,B,C,x,y);
    input  A,B,C;
    output x,y;
    wire e;
    and  #(30) g1(e,A,B);
    not  #(10) g2(y,C);
    or   #(20) g3(x,e,y);
endmodule
```



Verilog Example with Delay

```
// Description of circuit with delay
module circuit_with_delay (A,B,C,x,y);
    input  A,B,C;
    output x,y;
    wire e;
    and  #(30) g1(e,A,B);
    not  #(10) g2(y,C);
    or   #(20) g3(x,e,y);
endmodule
```


t=30:

events: e:0/1 x:1/0

simulations: g3(OR) e=1,y=0,t=20(50)

Verilog Example (Waveform)
 
```
// Description of circuit with delay
module circuit_with_delay (A,B,C,x,y);
    input  A,B,C;
    output x,y;
    wire e;
    and  #(30) g1(e,A,B);
    not  #(10) g2(y,C);
    or   #(20) g3(x,e,y);
endmodule
```



Verilog Example with Delay

```
// Description of circuit with delay
module circuit_with_delay (A,B,C,x,y);
    input  A,B,C;
    output x,y;
    wire e;
    and  #(30) g1(e,A,B);
    not  #(10) g2(y,C);
    or   #(20) g3(x,e,y);
endmodule
```

t=50:

events: x:0/1

simulations: NONE

Verilog Test Benches

- Only Used FOR SIMULATION
- Another Verilog Module that:
 - Provides Input
 - Allows Various Modules to be Interconnected
 - Contains Simulation Specific Commands
- Separation into Different Modules Important:
 - Can Synthesize Modules Directly
 - Can Change Abstraction of Modules
 - “Top-Level” Design
 - Allows Large Design Teams to Work Concurrently

Verilog Example with Testbench

```
// Stimulus for simple circuit
module stimcrct;
reg A, B, C;
wire x, y;
circuit_with_delay cwd(A, B, C, x, y);
initial
  begin
    A=1'b0; B=1'b0; C=1'b0;
    #100
    A=1'b1; B=1'b1; C=1'b1;
    #100    $finish;
  end
endmodule

// Description of circuit with delay
module circuit_with_delay (A,B,C,x,y);
  input  A,B,C;
  output x,y;
  wire e;
  and # (30) g1(e,A,B);
  not # (10) g2(y,C);
  or  # (20) g3(x,e,y);
endmodule
```

© 2002 Prentice Hall, Inc.
M. Morris Mano
DIGITAL DESIGN, 3e.

45

always and initial blocks

- Both Types of Blocks Contain Procedural (Sequential) Statements
- If More than One Procedural Statement use **begin - end**
- **Always** Block is Scheduled to Simulate/Execute at EVERY Simulation Time Cycle
- **Initial** Block is Scheduled to Simulate Only at the First Time Epoch

46

Verilog Simulation with Testbench

- Most Simulators Allow for Graphic Timing Diagrams to be Used
 - SynaptiCAD (software packaged with M. Mano textbook)
 - ModelTech (commercial simulator – free at www.model.com)
 - Cadence Verilog XL (commercial tool)
 - QuartusII (built-in timing simulator with Altera toolset)

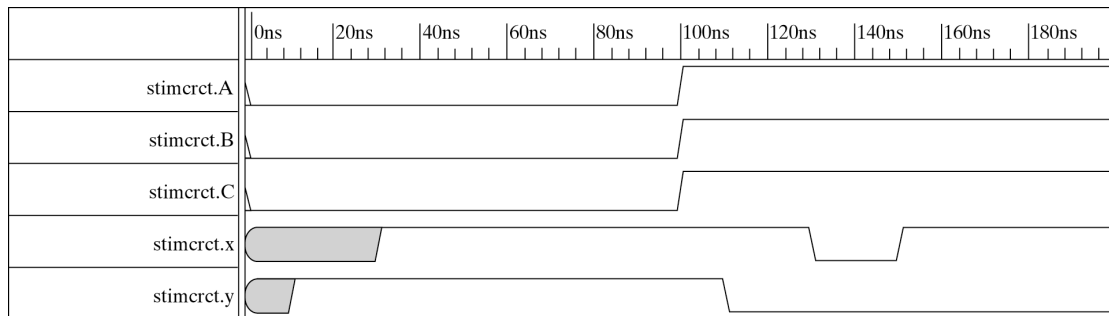


Fig. 3-38 Simulation Output of HDL Example 3-3

Model Abstractions in Verilog

- Netlist Level Models
 - Contain enough information to construct in lab
 - structural modeling
 - Commonly “Lowest” level of abstraction
 - Useful for Transfer Among CAD tools
- RTL (register transfer language) Level
 - Composed of Boolean Expressions and Registers
 - Can be Automatically Synthesized to a netlist
 - We will work mostly at this level
- Behavioral Level
 - High-level Constructs that only Describe Functionality
 - Automatic Behavioral Synthesis Tools do Exist